


Lecture 4

Physics 1402: Lecture 10 Today's Agenda


- **Announcements:**
 - Lectures posted on:
www.phys.uconn.edu/~rcote/
 - HW assignments, solutions etc.
- **Homework #3:**
 - On Masterphysics : due Friday at 8:00 AM
 - Go to masteringphysics.com

Electromotive force

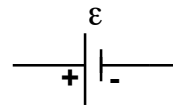- **Provides a constant potential difference between 2 points**
 - ϵ : “electromotive force” (emf)
- **May have an internal resistance**
 - Not “ideal” (or perfect: small loss of V)
 - Parameterized with “internal resistance” r in series with ϵ
- **Potential change in a circuit**




$$\epsilon - Ir - IR = 0$$

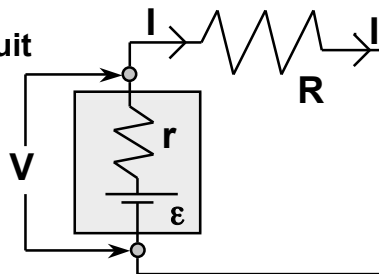

Lecture 4

Power

Batteries & Resistors

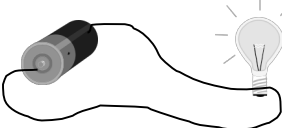

Rate is: $\frac{\text{energy}}{\text{time}} = \text{power} \left(\frac{J}{s} \right)$

What's happening?

Assert: $P = VI$

Energy "drop" per charge

For Resistors: $P = (IR)I = I^2R$ or $\frac{V^2}{R}$

Energy expended

chemical to electrical to heat

Charges per time

Batteries (non-ideal)

- Parameterized with "internal resistance" r in series with ϵ
- ϵ : "electromotive force" (emf) = $V(I=0)$


$$\epsilon - Ir = V$$

$$\epsilon - Ir - IR = 0$$

↓

$$I = \frac{\epsilon}{R + r}$$

⇒ $V = \epsilon \frac{R}{R + r}$

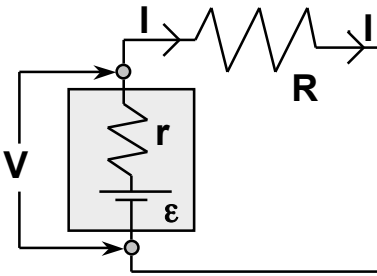


Power delivered to the resistor R:

$$P = I^2 R = \frac{\epsilon^2 R}{(R + r)^2}$$

P_{\max} when $R/r = 1$!

Lecture 4

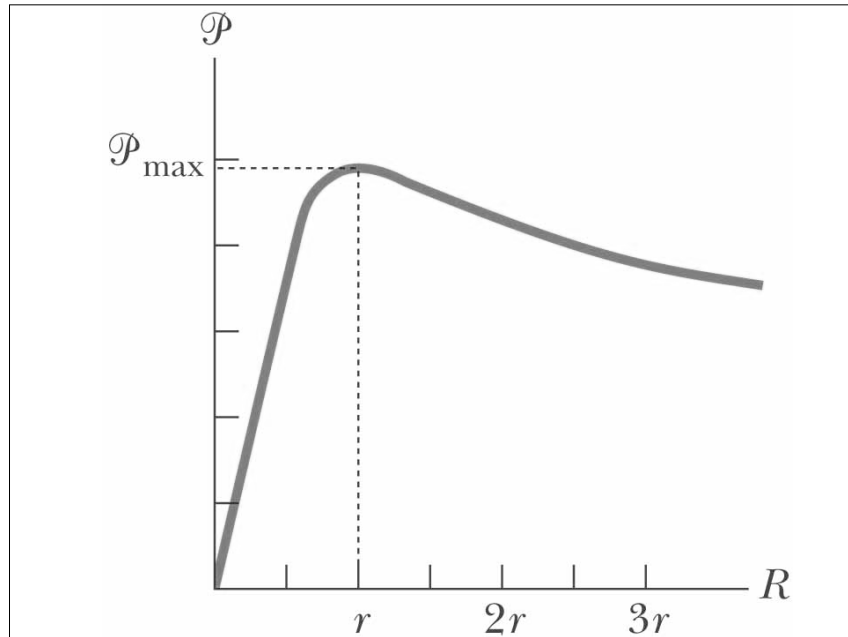

Devices

- **Conductors:**


Purpose is to provide zero potential difference between 2 points.

- » Electric field is never exactly zero.. All conductors have some resistivity.
- » In ordinary circuits the conductors are chosen so that their resistance is negligible.


- **Batteries (Voltage sources, seats of emf):**

Purpose is to provide a constant potential difference between 2 points.

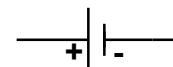- » Cannot calculate the potential difference from first principles.. electrical \leftrightarrow chemical energy conversion. Non-ideal batteries will be dealt with in terms of an "internal resistance".



OR

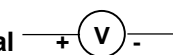

Lecture 4

Devices

- **Resistors:**



Purpose is to limit current drawn in a circuit.


- » Resistance can be calculated from knowledge of the geometry of the resistor AND the “resistivity” of the material out of which it is made.
- » The effective resistance of series and parallel combinations of resistors will be calculated using the concepts of potential difference and current conservation (Kirchoff's Laws).

- **Resistance**

Resistance is defined to be the ratio of the applied voltage to the current passing through.

$$R \equiv \frac{V}{I}$$

UNIT: OHM = Ω

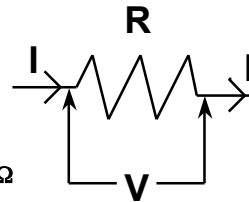

How resistance is calculated

- **Resistivity**

- property of all materials
- measures how much current density j results from a given electric field E in that material
- units are Ohm x m (Ωm)

$$\rho = \frac{E}{j}$$

- **Conductivity**

- sometimes used instead of resistivity
- measures the same thing as ρ

$$\sigma = \frac{1}{\rho}$$

- **Resistance**

- property of an object
- depends on resistivity of its material and its geometry

$$R = \frac{\rho L}{A}$$

- **Conductance**

- sometimes used instead of resistance
- measures the same thing as R

$$c = \frac{1}{R}$$

Lecture 4

Resistors in Series


The Voltage "drops":

$$V_a - V_b = IR_1 \quad V_b - V_c = IR_2$$
$$V_a - V_c = I(R_1 + R_2)$$

Whenever devices are in **SERIES**, the current is the same through both!


This reduces the circuit to:

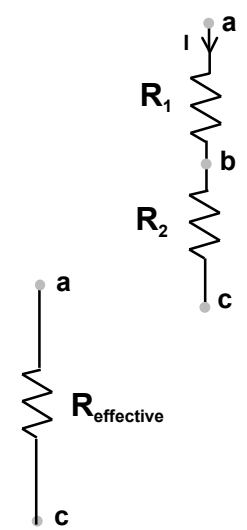Hence: $R_{\text{effective}} = R_1 + R_2$



Another (intuitive) way...

Consider two cylindrical resistors with lengths L_1 and L_2
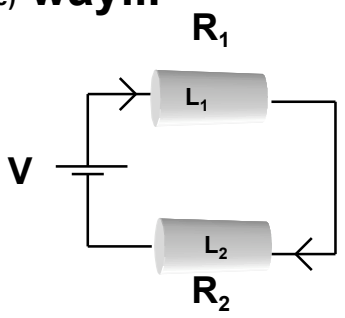
$$R_1 = \frac{\rho L_1}{A}$$
$$R_2 = \frac{\rho L_2}{A}$$


Put them together, end to end to make a longer one...

$$R_{\text{effective}} = \rho \frac{L_1 + L_2}{A} = R_1 + R_2$$

$R = R_1 + R_2$

Lecture 4

Resistors in Parallel

- What to do? $V = IR$
- Very generally, devices in parallel have the same voltage drop

- But current through R_1 is not I !
Call it I_1 . Similarly, $R_2 \leftrightarrow I_2$.



$$V = I_1 R_1$$

$$V = I_2 R_2$$

- How is I related to I_1 & I_2 ??
Current is conserved!

$$I = I_1 + I_2$$
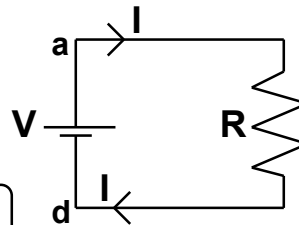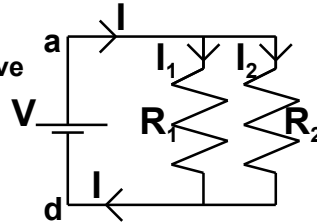
$$\Rightarrow \frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} \Rightarrow \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$




Another (intuitive) way...

Consider two cylindrical resistors with cross-sectional areas A_1 and A_2

$$R_1 = \frac{\rho L}{A_1}$$

$$R_2 = \frac{\rho L}{A_2}$$

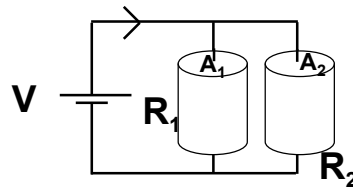

Put them together, side by side ... to make a "fatter" one with $A=A_1+A_2$,

$$R_{\text{effective}} = \frac{\rho L}{A_1 + A_2} \Rightarrow \frac{1}{R_{\text{effective}}} = \frac{A_1}{\rho L} + \frac{A_2}{\rho L} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\Rightarrow \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$


Lecture 4

Summary

- **Resistors in series**

- the current is the same in both R_1 and R_2
- the voltage drops add


$$R = R_1 + R_2$$

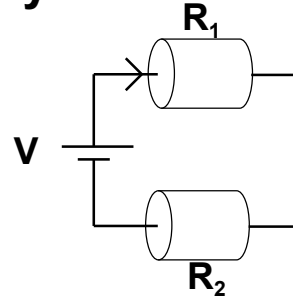


- **Resistors in parallel**

- the voltage drop is the same in both R_1 and R_2
- the currents add
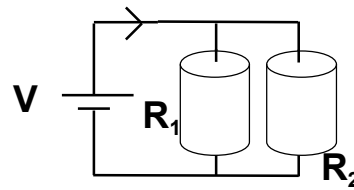
$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$



Lecture 10, ACT 1

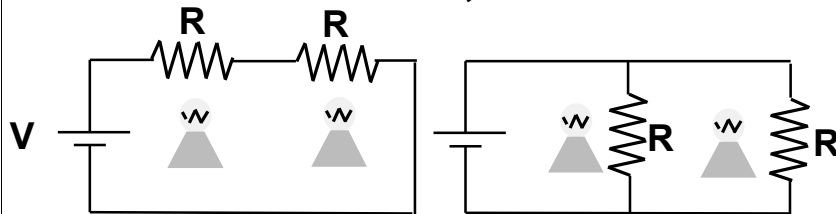


- I have two identical light bulbs. First I hook them up in series. Then I hook them up in parallel. In which case are the bulbs brighter? (The resistors represent light bulbs whose brightness is proportional to $P = I^2R$ through the resistor.)

A) Series

B) Parallel

C) The same

Lecture 4

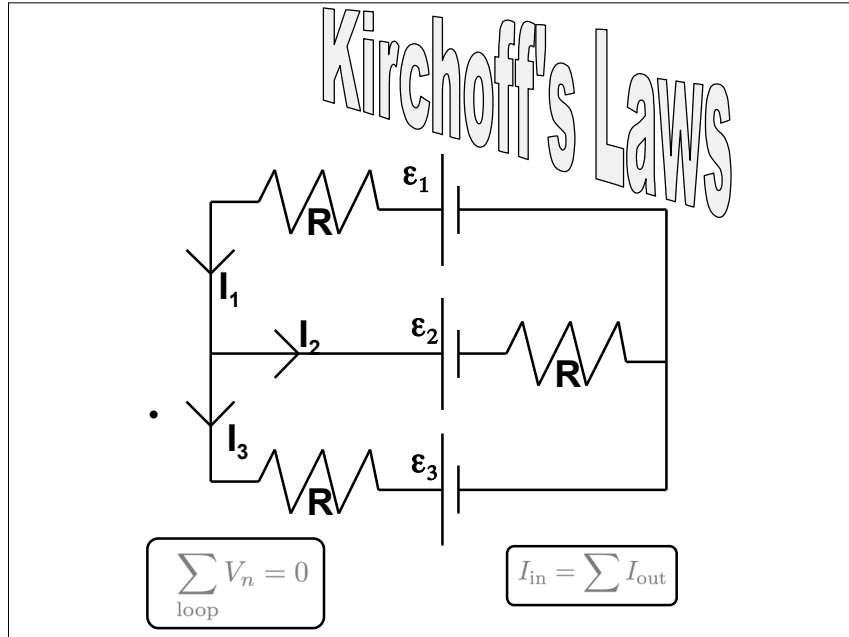

Kirchoff's First Rule


"Loop Rule" or "Kirchoff's Voltage Law (KVL)"

"When any closed circuit loop is traversed, the algebraic sum of the changes in potential must equal zero."

KVL: $\sum_{\text{loop}} V_n = 0$


- This is just a restatement of what you already know: that the potential difference is independent of path!
- RULES OF THE ROAD:

We will follow the convention that voltage gains enter with a + sign and voltage drops enter with a - sign in this equation.

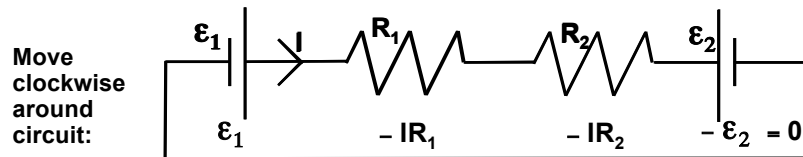

Lecture 4

Loop Example

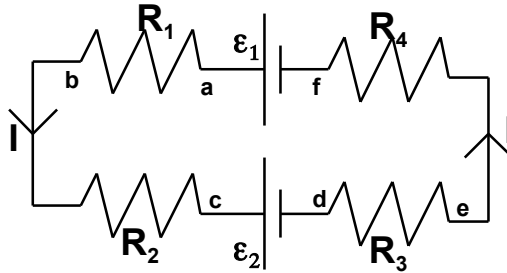


KVL: $\sum_{\text{loop}} V_n = 0 \Rightarrow -IR_1 - IR_2 - \varepsilon_2 - IR_3 - IR_4 + \varepsilon_1 = 0$

$$\Rightarrow I = \frac{\varepsilon_1 - \varepsilon_2}{R_1 + R_2 + R_3 + R_4}$$



Lecture 10, ACT 2

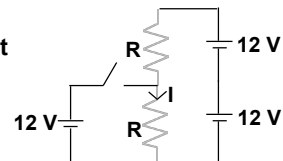- Consider the circuit shown.
 - The switch is initially open and the current flowing through the bottom resistor is I_0 .
 - After the switch is closed, the current flowing through the bottom resistor is I_1 .
 - What is the relation between I_0 and I_1 ?



(a) $I_1 < I_0$

(b) $I_1 = I_0$

(c) $I_1 > I_0$

Lecture 4

Kirchoff's Second Rule

"Junction Rule" or "Kirchoff's Current Law (KCL)"

- In deriving the formula for the equivalent resistance of 2 resistors in parallel, we applied Kirchoff's Second Rule (the junction rule).

"At any junction point in a circuit where the current can divide (also called a node), the sum of the currents into the node must equal the sum of the currents out of the node."

$$I_{\text{in}} = \sum I_{\text{out}}$$

- This is just a statement of the conservation of charge at any given node.
-