




Parallel RCL Circuit

PHYSICS 258/259 D.S. Hamilton

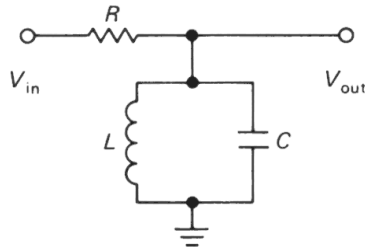Problem

Obtain the complex transfer function $\mathbf{H}(f)$ for the circuit shown below over the range $0 < f < \infty$. Plot the magnitude of \mathbf{H} and the phase angle as a function of frequency on a log scale.



The figure is a simple four-terminal RCL tank circuit. The inductor has a series resistance R_L and the capacitor has a parallel resistance R_C .

Parameters

$$L := 22.0 \cdot \text{mH} \quad C := 0.015 \cdot \mu\text{F} \quad R := 39 \cdot \text{k}\Omega$$

$$R_L := 15 \cdot \Omega \quad R_C := 100 \cdot \text{M}\Omega$$

Solution

The complex transfer function can be written down by inspection using our previous Mathcad worksheet on the LC circuit.:

$$Z_{LC}(f) := \left[(j \cdot 2 \cdot \pi \cdot f \cdot L + R_L)^{-1} + R_C^{-1} + j \cdot 2 \cdot \pi \cdot f \cdot C \right]^{-1} \quad Z(f) := R + Z_{LC}(f)$$

$$H(f) := \frac{Z_{LC}(f)}{Z(f)}$$



Parameters for plotting



$$f_0 := \frac{1}{2 \cdot \pi \cdot \sqrt{L \cdot C}} \quad f_0 = 8.761 \cdot 10^3 \text{ s}^{-1} \quad |H(f_0)| = 0.715$$

$$f_{\text{low}} := .01 \cdot f_0 \quad f_{\text{high}} := 100 \cdot f_0$$

$$N := 800 \quad i := 0..N - 1$$
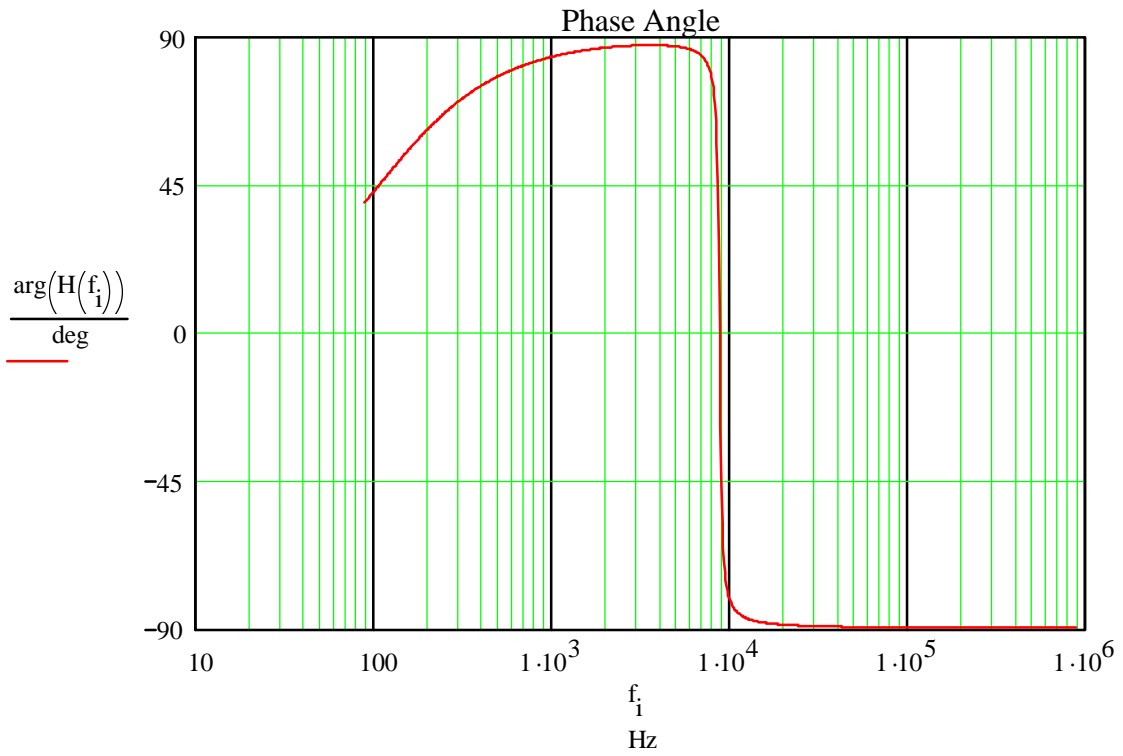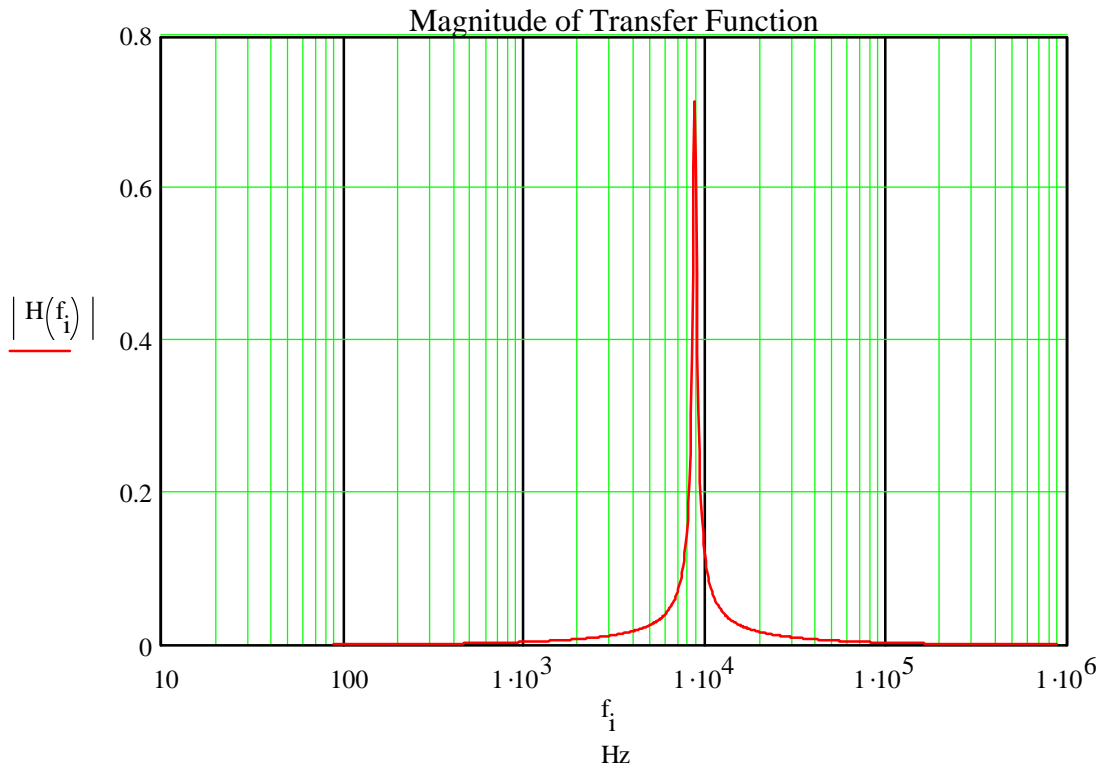
$$r := \log\left(\frac{f_{\text{low}}}{f_{\text{high}}}\right) \cdot \frac{1}{N} \quad r = -5 \cdot 10^{-3} \quad f_i := f_{\text{high}} \cdot 10^{i \cdot r}$$



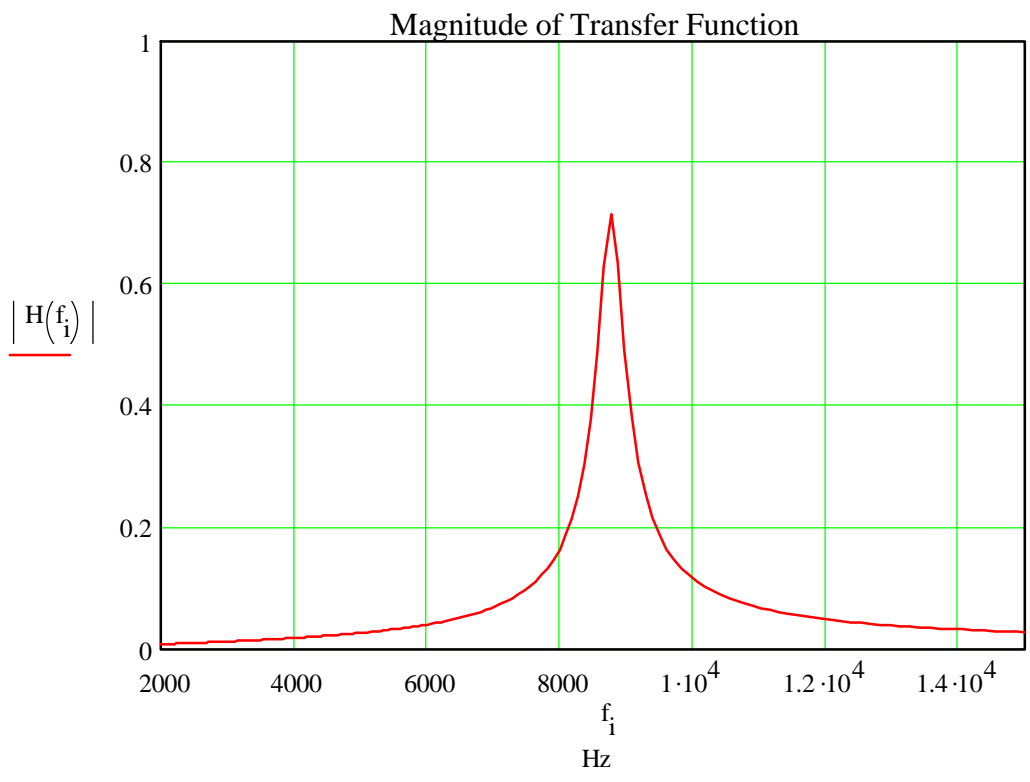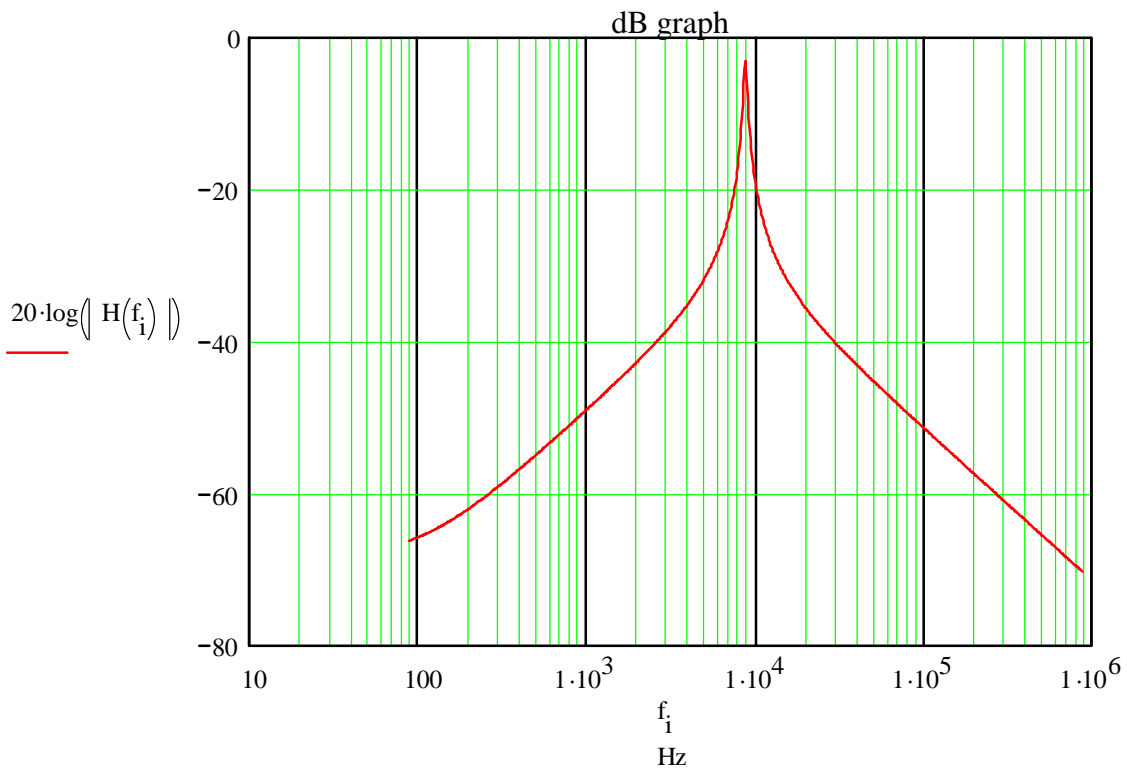

$$Q := 2 \cdot \pi \cdot f_0 \cdot R \cdot C \quad Q = 32.203 \quad \frac{1}{Q} = 0.031$$

$$\Delta f_{3\text{dB}} := \frac{f_0}{Q} \quad \Delta f_{3\text{dB}} = 272.06 \text{ s}^{-1}$$