



High-Pass RC Circuit


PHYSICS 258/259 D.S. Hamilton

Introduction

A high-pass filter will pass the high-frequency Fourier components, but not those components at lower frequencies.

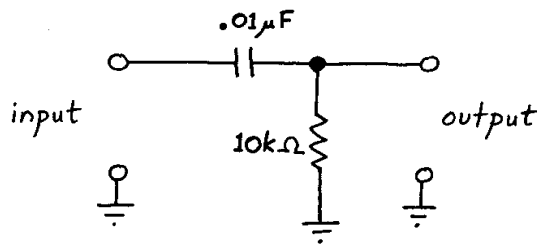Problem

Obtain the complex transfer function $H(\omega)$ for the circuit shown below over the range $0 < \omega < \infty$. Plot the magnitude of H and the phase angle as a function of ω on a log scale.



The figure is simple four-terminal RC high-pass filter.

Parameters

$$C := 0.01 \cdot \mu\text{F}$$

$$R := 10 \cdot \text{k}\Omega$$

Solution

The complex transfer function can be written down by inspection:

$$H(\omega) := \frac{R}{R + \frac{1}{j \omega \cdot C}}$$

Parameters for plotting

characteristic frequency: $\omega_0 := \frac{1}{R \cdot C}$ $\omega_0 = 1 \cdot 10^4 \text{ s}^{-1}$

Low/High values to plot: $\omega_{\text{low}} := .001 \cdot \omega_0$ $\omega_{\text{high}} := 100 \cdot \omega_0$

Number of points: $N := 400$ $i := 0..N - 1$

Step size: $r := \log\left(\frac{\omega_{\text{low}}}{\omega_{\text{high}}}\right) \cdot \frac{1}{N}$ $r = -0.012$

Range variable: $\omega_i := \omega_{\text{high}} \cdot 10^{i \cdot r}$

