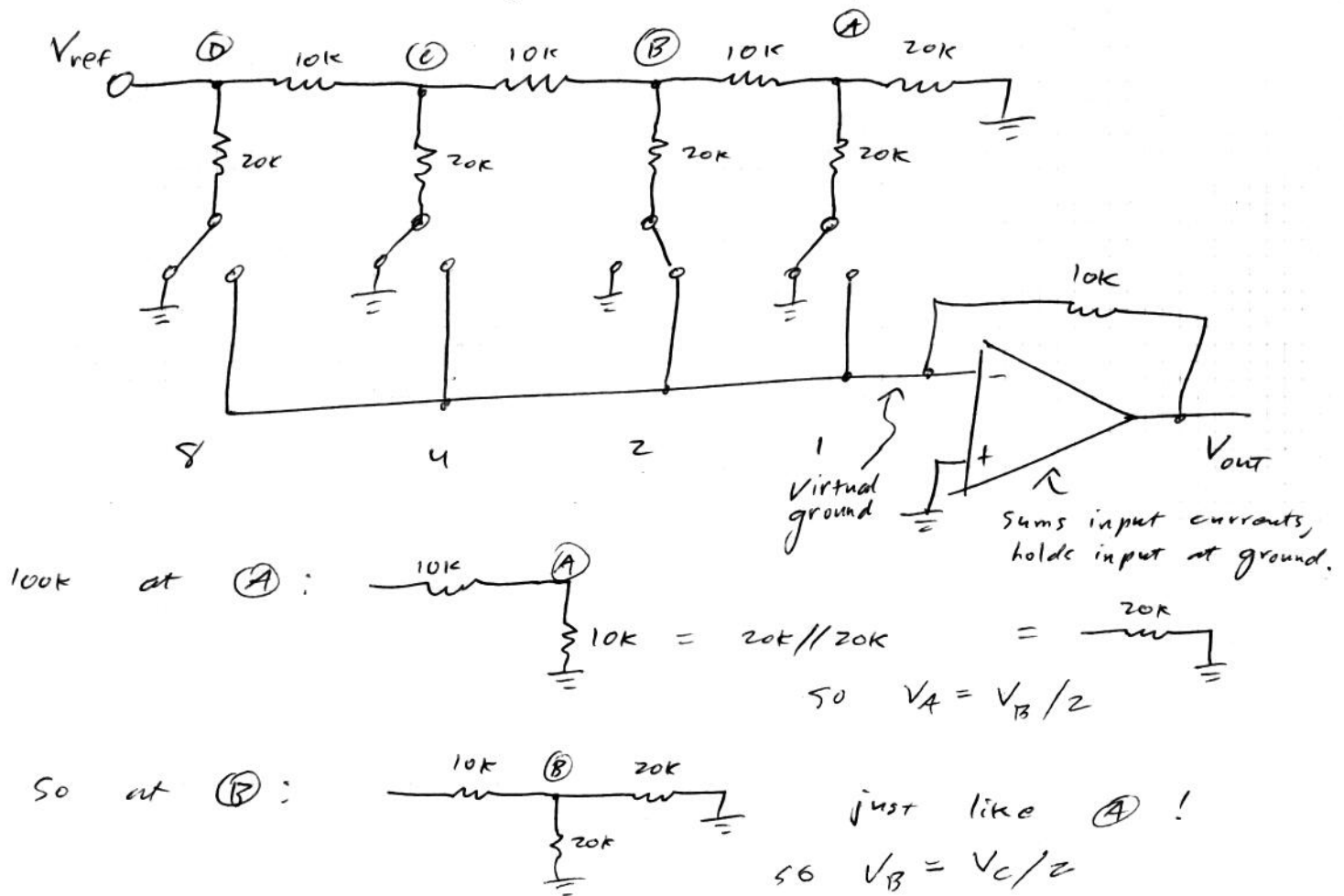


D/A and A/D conversion

How to get back and forth?

DAC is easy in principle. Use digitally-controlled analog switches to switch a resistor ladder. Usual approach is R-2R ladder:




Thus regardless of switch settings, $V_D = 2V_C = 4V_B = 8V_A$

Now all we do is switch the current into an op amp.


As shown, V_B is switched in with a gain of $\frac{1}{2}$,

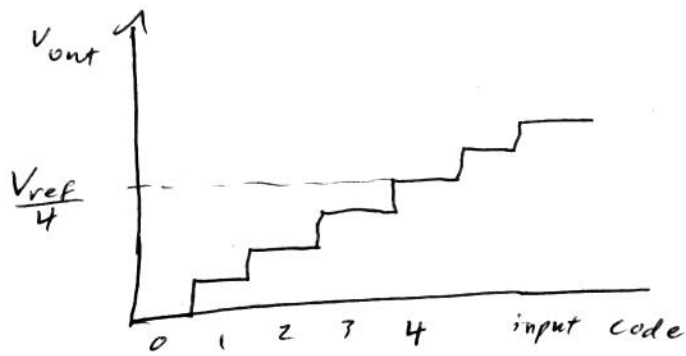so $V_{out} = \frac{1}{8} V_{ref}$. Switch (D) gives $\frac{1}{2} V_{ref}$, etc.



← watch specs --
integral & diff'l linearity,
monotonicity.
← vital if
feedback !!

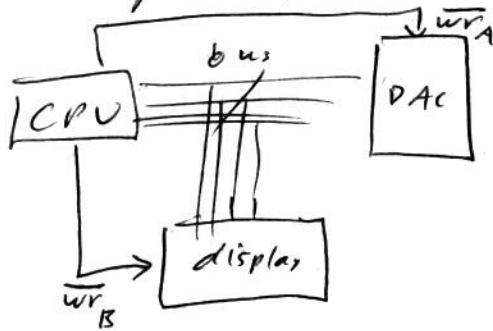Many DAC's have a resistor ladder with current outputs; used directly or with op amps. Often has input latches as well -- allows shared data lines:



Example: ~~8405~~ DAC0831,
only D3 to D4.


For microcontrollers, MCP4822
has fast SPI serial interface --
2x12 bits in 8-pin package for ~\$3.

Used for generating waveforms, controlling instruments,
heaters, ... ad infinitum.

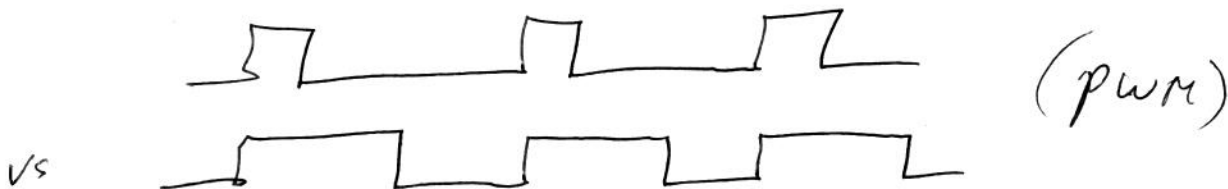6-18 bit converters can be had on chips.

There's also another approach -- averaging DAC.

Switch system on & off with varying duty cycle --




Allows good control of slow systems (e.g., room heat.)
Can even average pulse train with an RC filter, but
not as common.

ADC's :



Many methods.

1) One simple & oft-neglected one is:

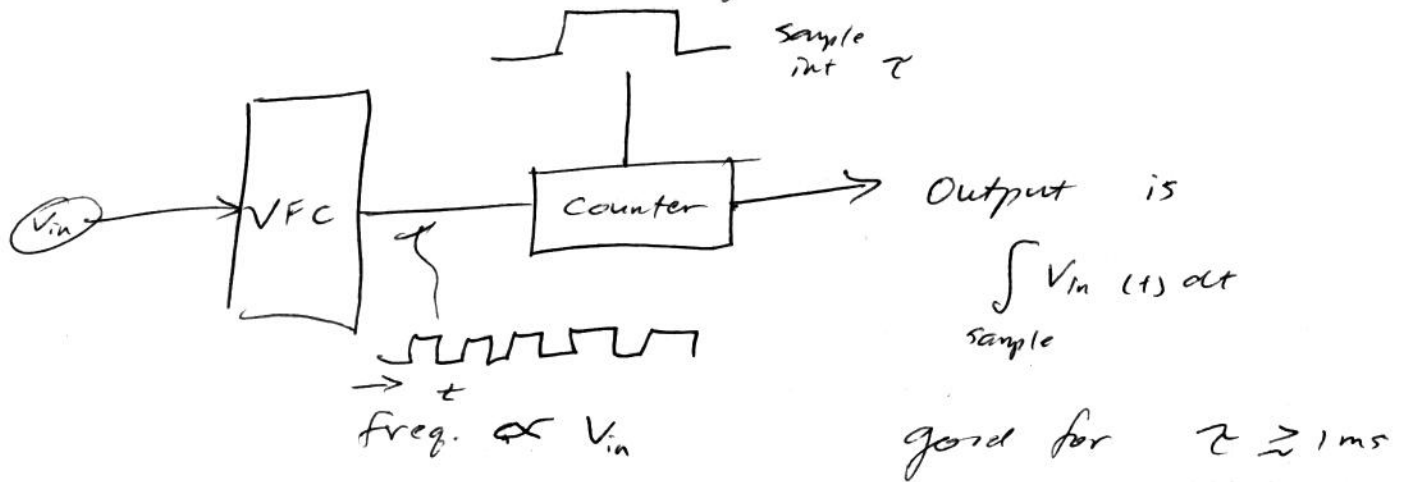


Easy to build with full control over integration period.

2) successive approximations

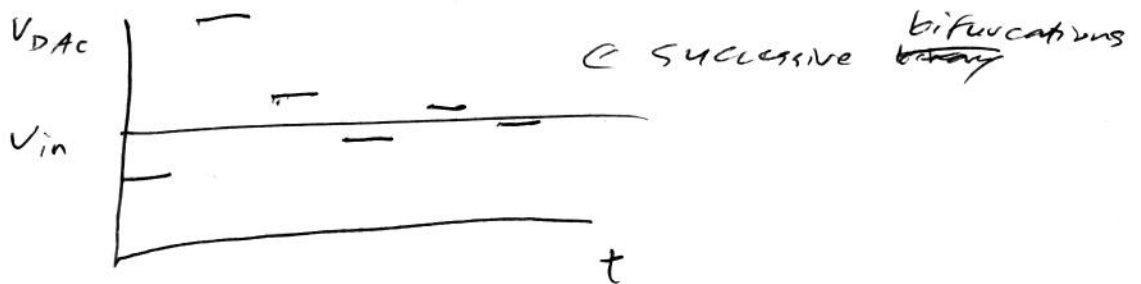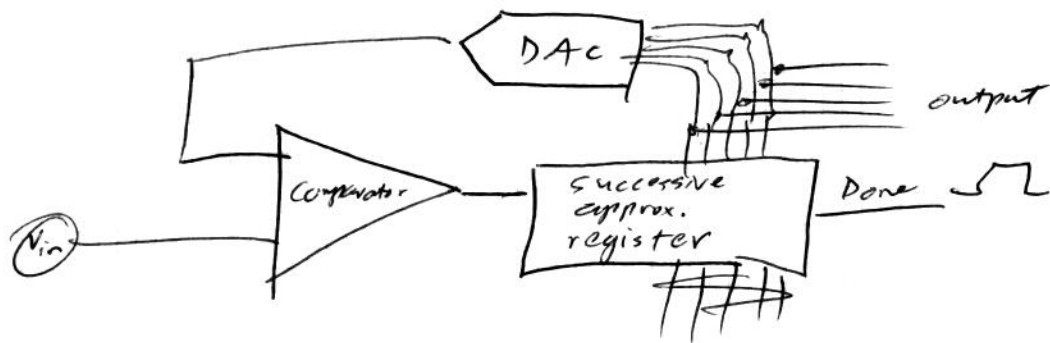

For n bits, need n DAC settling times
 $\Rightarrow 1 \mu\text{s}$ to $50 \mu\text{s}$ typ.


3) RC integration:

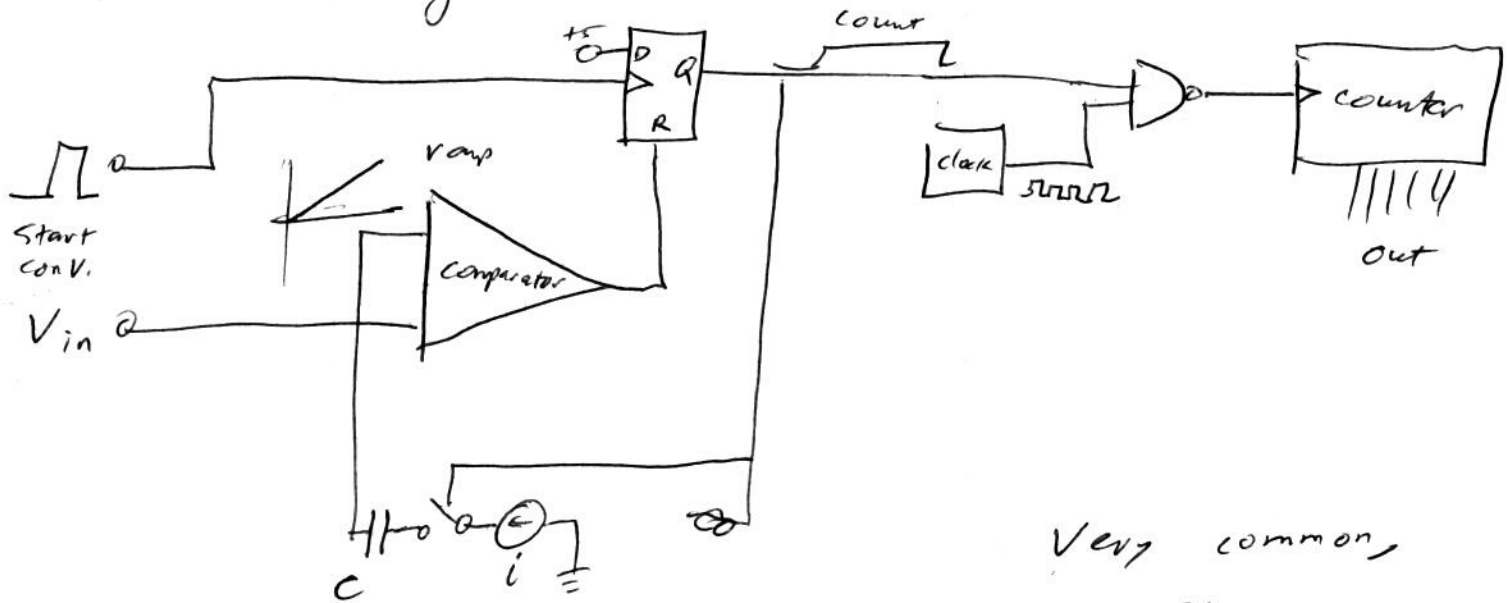

Very common,


Slow but
precise,

Always monotonic.
(like VFC)

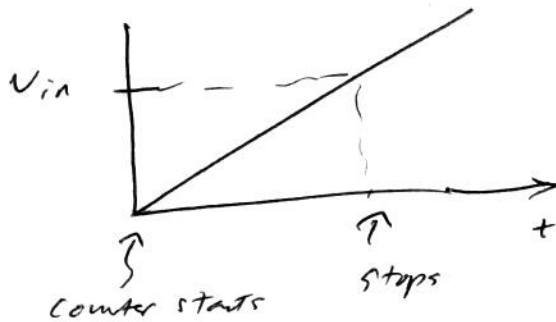

"Dual slope" version works better. A more elaborate variation is the "delta sigma" converter, with digital averaging.


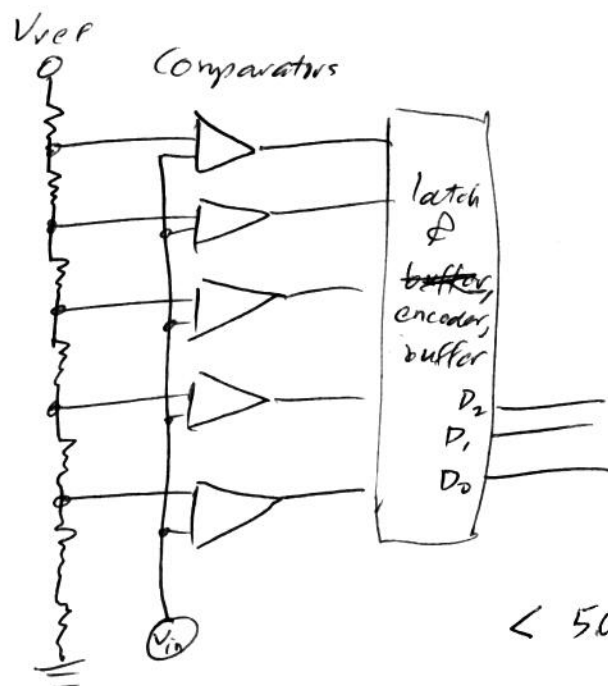
4) Direct "flash" conversion (digital scopes, etc.)



binary output.

< 50 psec is possible!

Sample & Hold amplifier

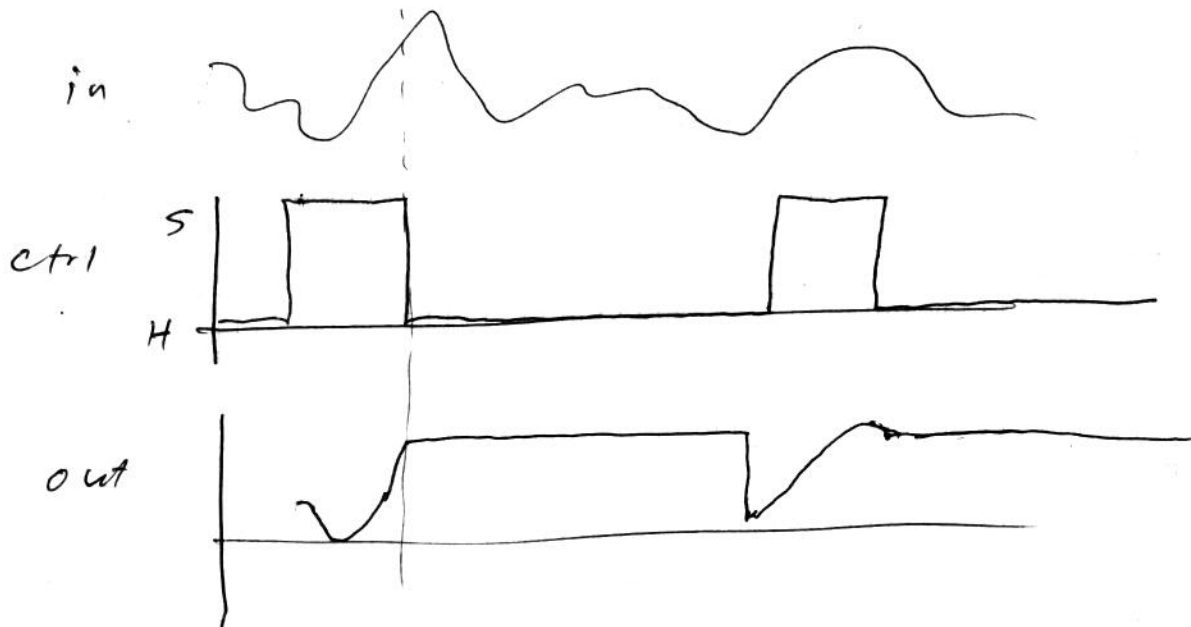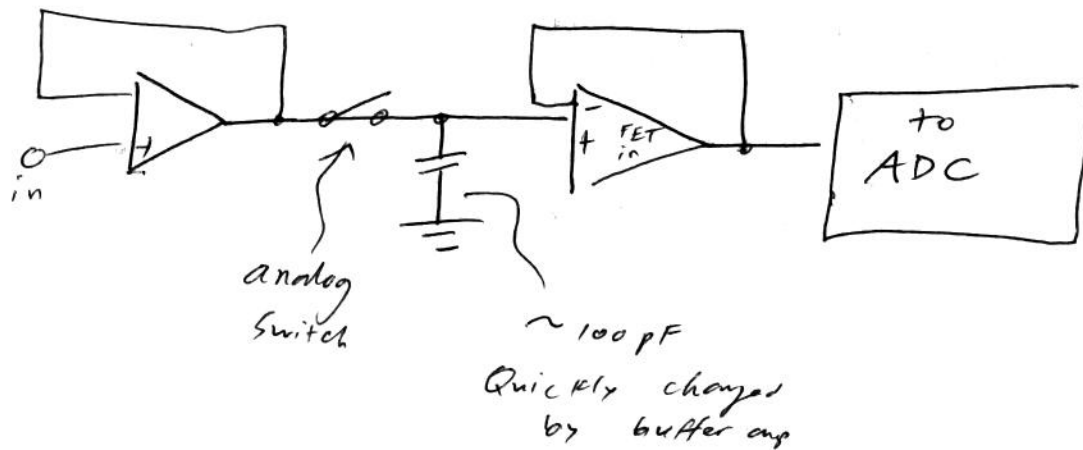


This waveform is undersampled.

Droop is caused by I_{sc2} , $I = C \frac{dV}{dt}$.
 (Bigger C takes longer to charge.)


PLL's

another digital-analog hybrid.

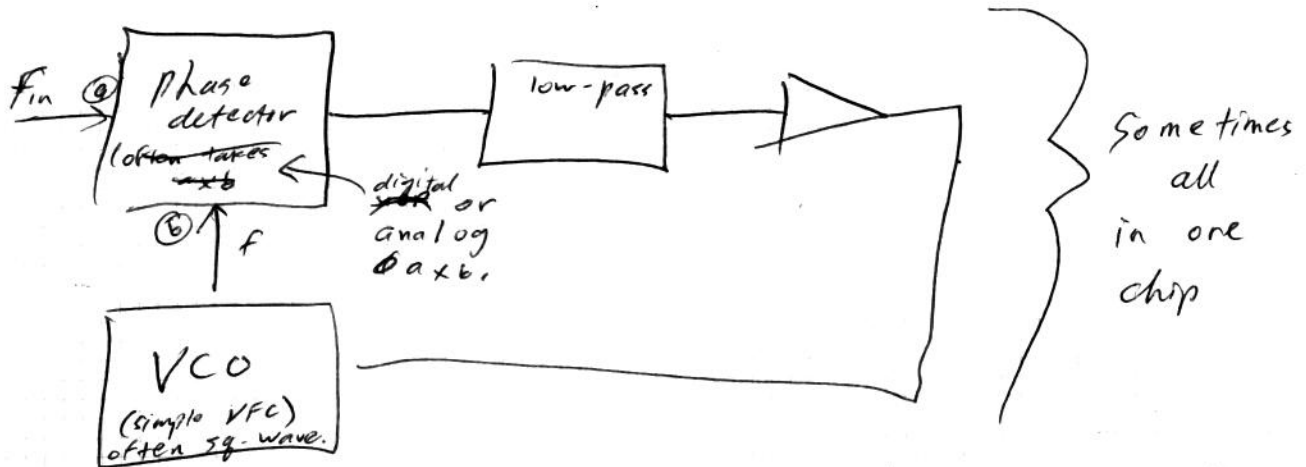- AM & FM de-modulators
- Freq. synthesis
- Harmonic generation
- Synchronization of noisy signals



Standard use is ntx harmonic lock

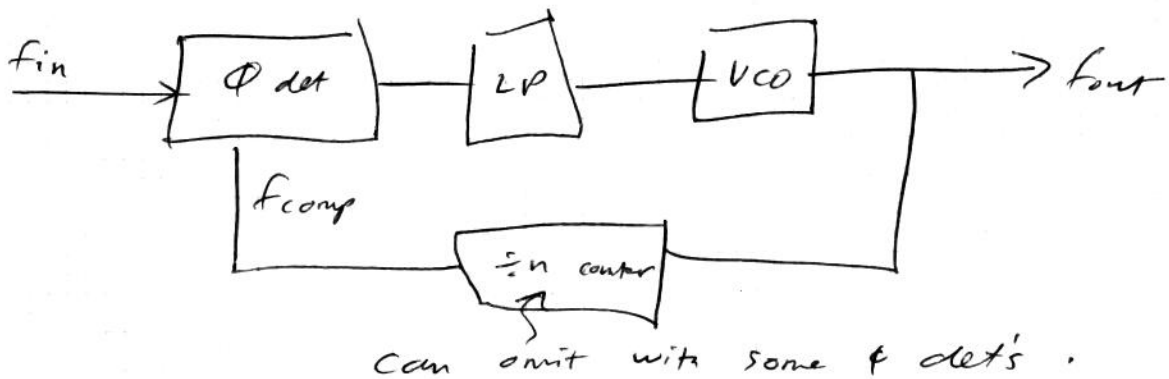See texts and web for lots more.Simplest ϕ det is an XOR gate

always ~~false~~ true } take time average to get $\Delta\phi$.

“ ~~false~~ true }

Finally, it's worth mentioning mechanical ADC's --

Example: shaft encoders: alternative to pot. + 8-bit ~~DAC~~ ^{ADC}:



Commonly get ≈ 256 pulses/revolution in commercial units.

Some elaborate encoding schemes ~~can~~ ^{can} be used to get μ rad control of rotation in motor driven applications --- replaces old stepper or synch. schemes.

Used in most new 'scopes, other good μ p - controlled instruments.