

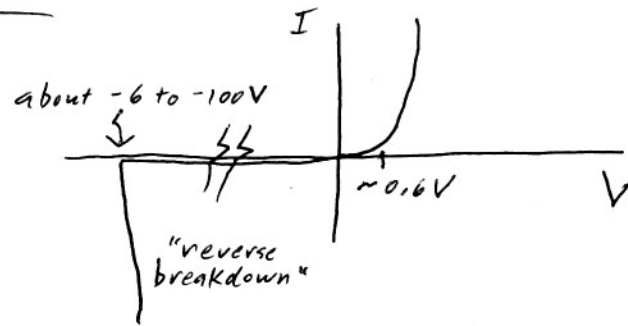


Diodes

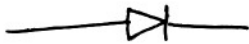

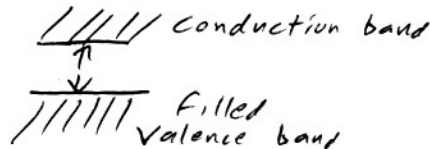For Si (Ge, GaAs similar) there is a bandgap $\approx kT$:




$$\frac{kT}{e} \approx 0.025V \text{ at room temp.}$$


There are just a few thermal conduction electrons,
 $\sim 10^{16} \text{ m}^{-3}$ at room temp.

Things change drastically if trace impurities are added:

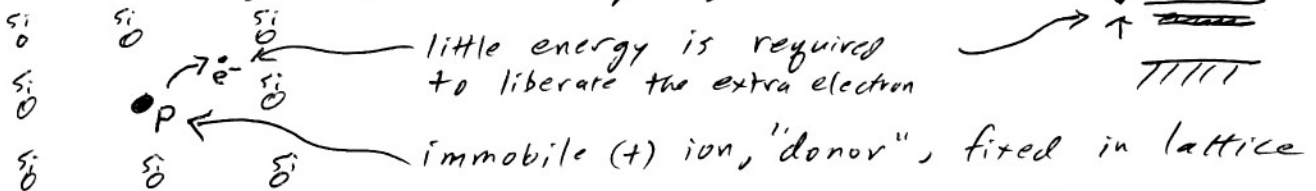n-type: Add P, As, or Sb dopant, valence 5




p-type: Add B, valence 3, or similar

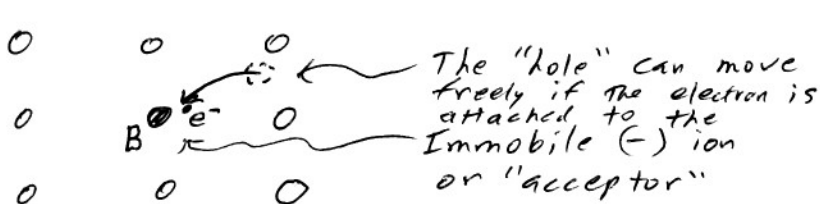


So in effect, p-type charge carriers are (+).

Diode junction

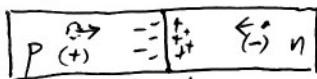

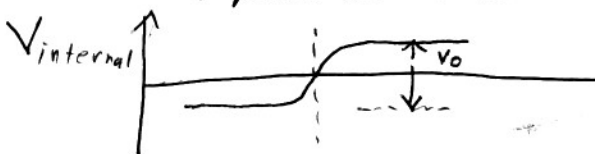depletion region builds a potential barrier



Holes and electrons recombine at boundary until the potential inhibits further net motion.

For Si, $V_0 \sim 0.5V$ (on the order of the bandgap)

Symbol

Equilibrium: Let N_p = hole density, N_e = electron density
 For holes on n side, no barrier, but very few holes are available. For holes on p side, fraction able to cross is given by a Boltzmann factor,


$$e^{-eV_0/k_B T} \quad (k_B T \sim \frac{1}{40} \text{ eV at } 300\text{K})$$

So in equilibrium,

$$N_p(\text{n side}) = N_p(\text{p side}) e^{-eV_0/k_B T}$$

$$\text{Likewise, } N_e(\text{p side}) = N_e(\text{n side}) e^{-eV_0/k_B T}$$

Externally biased diode

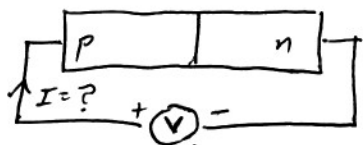

V will appear across depletion region, reducing potential to $V_0 - V$ (or increasing, if V is $(-)$).

Net flow of e^- from n side is now

$$I_e \propto N_e(\text{n side}) e^{-e(V_0 - V)/k_B T} - N_e(\text{p side})$$

$$\underbrace{\hspace{1.5cm}}_{\text{still } \approx N_e(\text{p side}) e^{eV_0/k_B T}}$$

$$= \underbrace{C N_e(\text{p side})}_{\equiv I_{e0}} (e^{eV/k_B T} - 1)$$

$\equiv I_{e0}$, electron saturation current

$$\text{So } I_e = I_{e0} (e^{eV/k_B T} - 1)$$

Similarly, $I_p = I_{p0} (e^{eV/k_B T} - 1)$, so altogether,

$$I \approx I_0 (e^{eV/k_B T} - 1). \quad \text{Also OK for reverse bias!}$$

A slightly modified version works better,

$$\boxed{I_{\text{diode}} \approx I_0 \left(e^{\frac{eV}{n k_B T}} - 1 \right)}$$

Here n is between 1 and 2, and accounts for recombination and other device-dependent effects.

This works well unless V is so negative that reverse avalanche breakdown occurs (failure!) or, in special "Zener diodes", a sharp breakdown is reached due to quantum tunneling. These are used as voltage references.

Where $\frac{e}{kT} \approx \frac{1}{.025V}$ as before assuming $T \approx 300K$.

and I_0 = "reverse saturation current", typ. $\sim 1\mu A$ or less.

and n contains device physics; it's about 1-2.

I_0 is set by flow of "minority" carriers.



← reverse breakdown occurs by

1) avalanche breakdown

or 2) Zener breakdown -- direct breakage of covalent bonds by E field at junction.

Normally causes destruction, but used intentionally for "zener diodes."

Ratings:

- Important ones are --
- 1) PIV (peak inverse voltage) or V_R (max)
 - 2) max. fwd current or I_F
 - 3) Reverse leakage I_R (max) (goes up 6.2% / $^{\circ}C$!)

Small-signal:

1N914: V_R (max) = 75V
(or 1N4148) I_F = 10 mA (cont.)^{max}, at $V_F = 0.75V$
 I_R (max) = 5 μA at $100^{\circ}C$ and V_R

Typ. rectifier:

1N4007: V_R (max) = 1000V
 I_F = 1000 mA (cont.), at $V_F = 0.9V$
 I_R (max) = 50 μA

Note: 1N400x is much slower than 1N914.

General rule: when "conducting", $\Delta V \sim 0.6V$
(of thumb) for Si diodes.



Still OK: ~~network~~ Kirchhoff's laws

Not OK: { Ohm's law (assumes linearity)
Thevenin's Theorem (assumes both linearity & superposition princ.)


Applications:

1) Rectification:



$$V_1 - V_2 = V_{in}$$

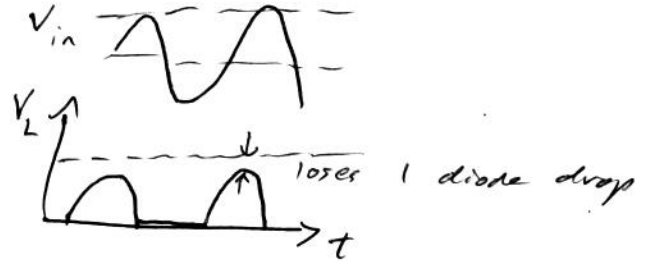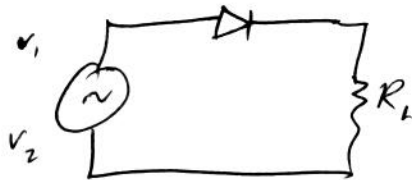

a) half-wave

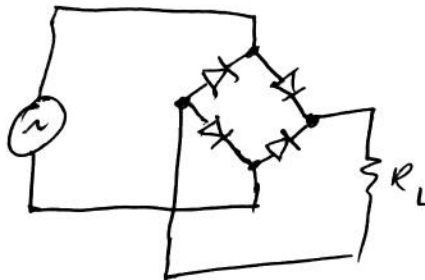



b) full-wave

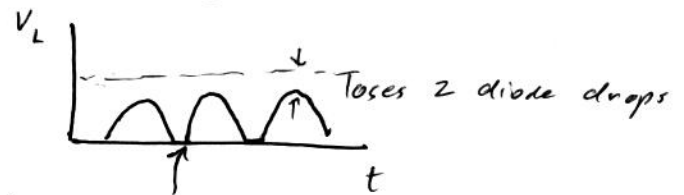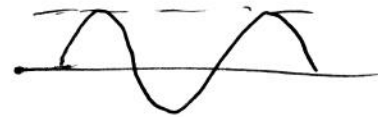

tiny omission due to diode drops.

Simple power supply:

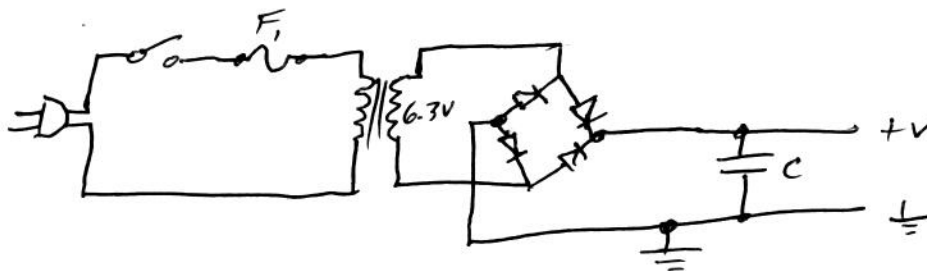

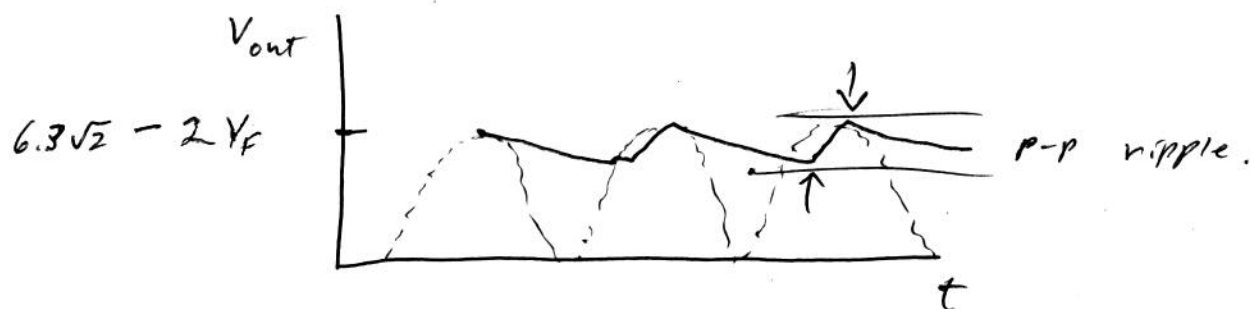

Estimate ripple: Look at limit of small ripple -

Assume $I_{load} \approx \text{constant}$, and that C discharges for full half-cycle, $\Delta t = \frac{1}{2f}$

$$\text{Then } \Delta V = \frac{Q}{C} = \frac{I_L \Delta t}{C} = \frac{I_{Load}}{2fC}$$

(This overestimates real ripple.)

Ex: $100 \mu F$, $I = 100 \text{ mA}$, 60 Hz



$$\Rightarrow \frac{.1}{2(60)(10^{-4})} = 8.3 \text{ V (!)}$$

So we need at least $1000 \mu F$ to do at all well, here. Apart from using huge capacitors (and xformers!),

a good solution is to add regulators and series inductors, called "chokes".

Increasing f also an option -- used by switching power supplies.

2) Variant: voltage doubler:

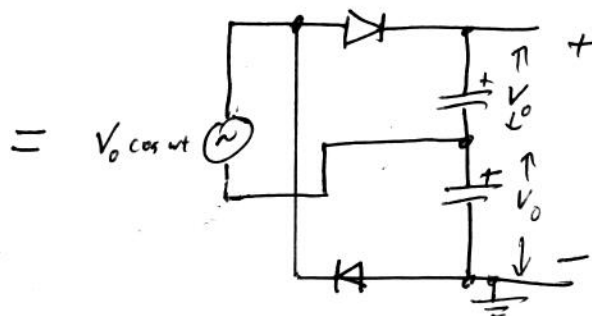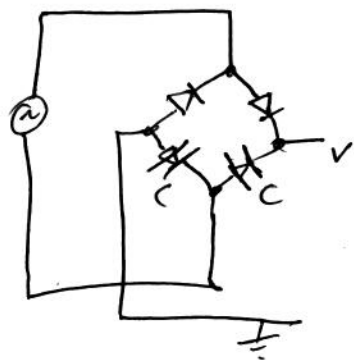




like 2 half-wave rectifiers in series.

Can extend for tripler, etc.

Diode clamps & limiters:

D-6


Basic clamp:

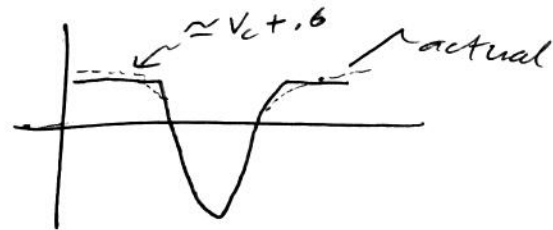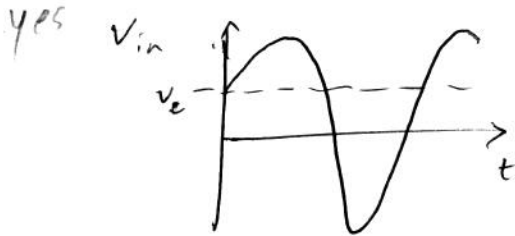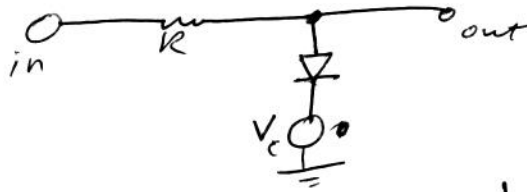

Want a perfect clamp? Use an op amp!


- Uses:
- 1) protection (e.g. in IC's)
 - 2) prevent overmodulation (radio, etc.)
 - 3) limit swing in servo, etc., prevent latching.

Symmetric limiter:

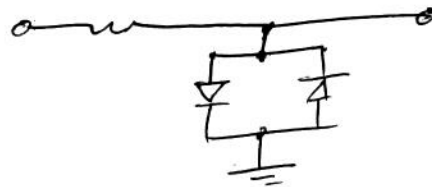


Also good for ampl. protection!

Variation -- dc restoration/shifting

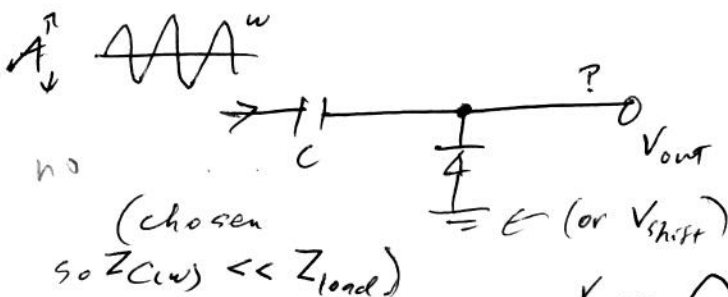


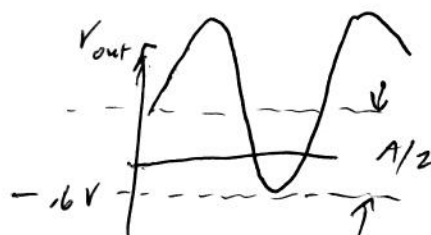When diode conducts, C charges. So its voltage builds up until conduction stops:




Zero is shifted by $\frac{A}{2} (-0.6V)$

Protection from back-emf:

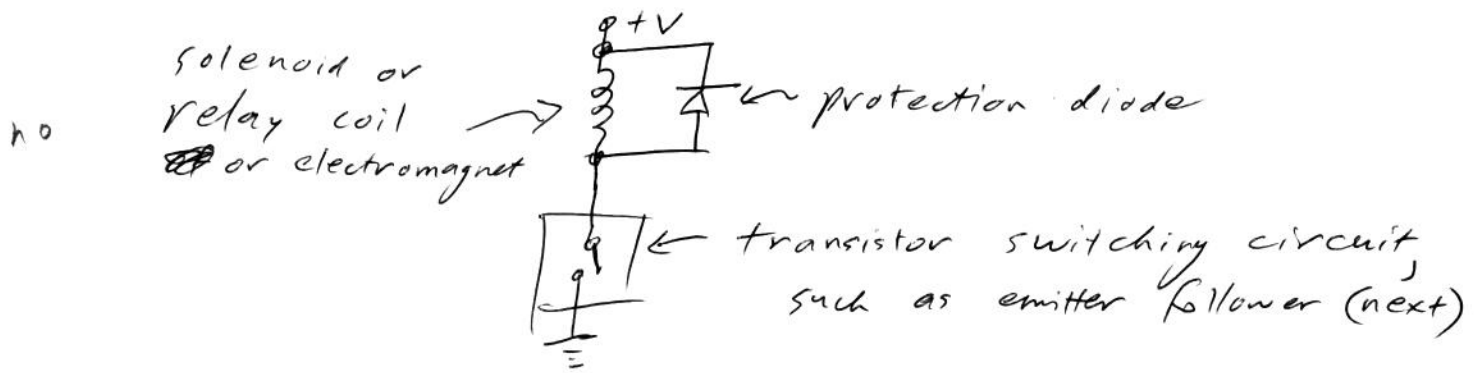

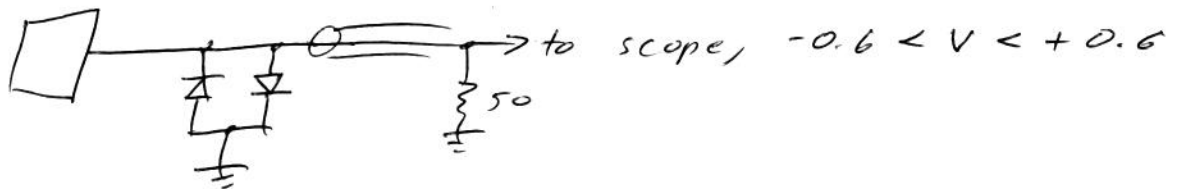For detectors with small signals, can even use




Diode Mixers & such:

D-8

Can explicitly exploit nonlinearity as a log converter.

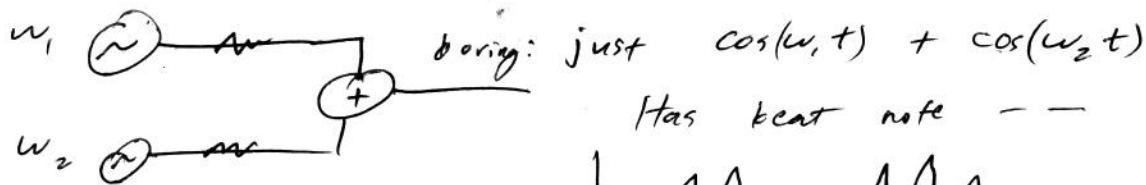Or can exploit it to generate new freq's --
See lab!



Has beat note --



yes

But replace $\oplus$ with  $V_{out} = IR = I_0 (e^{V/A} - 1) R$,
where $V = V_1 \cos w_1 t + V_2 \cos w_2 t$

To get



Has new freq's ---

$$e^{V/A} \sim \frac{V}{A} + \frac{1}{2} \left(\frac{V}{A} \right)^2 + \dots$$

gives $w_1 + w_2, 2w_1, \dots$

Can see $w_1 - w_2$ here in avg.

To reduce distortion, bias diode into conduction.

If $w_1 \ll w_2$, this is an amplitude modulator;

if comparable, it's a mixer.