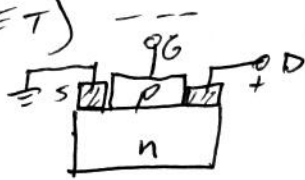


FET's come in several Flavours. Look first at an n-channel depletion mode junction FET (JFET)




(source, gate, drain)

1) $\rightarrow$ conductor.


IF $V_G = 0$, get limited conduction depending on V_{DS} .

IF $V_G < 0$,
(no gate current!)

$Z_{in} \rightarrow \infty$!

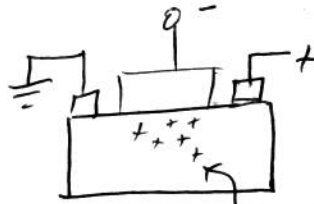

depleted region -- e^- are driven away.

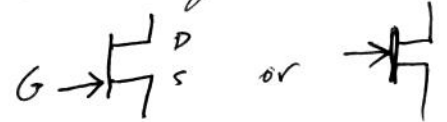


IF V_{DS} small, effect is to vary resistance R_{DS} with V_G


IF V_{DS} large ($> \text{few V}$), get complete depletion $\rightarrow I_{DS}$ is limited to a value determined by V_G (good for amplifier use)

So we need two types of plot:

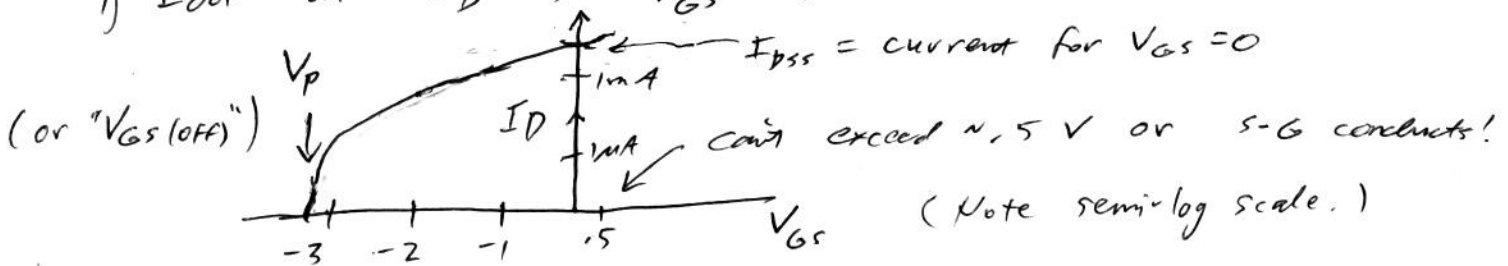1) Look at I_D vs V_{GS} for a fixed V_{DS} ---



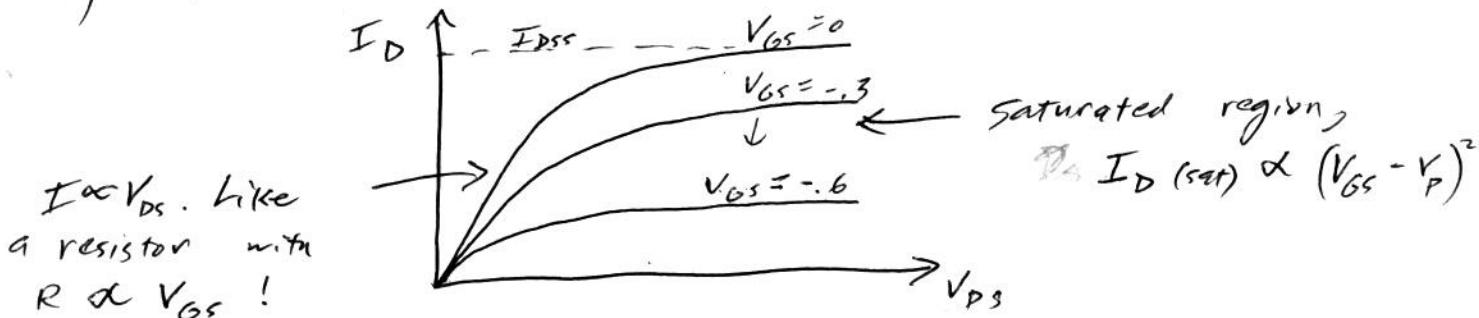2) look at I_D vs V_{DS} for various V_{GS}



Saturation occurs when depletion blocks the channel completely. So we can use device either as a variable resistor,

$$I_D = 2k \left((V_{GS} - V_P) V_{DS} - \frac{V_{DS}^2}{2} \right) \quad \text{or } V_T \text{ for enh. mode} \quad \textcircled{1} \quad (\text{low } V_{DS})$$

resistance "linear"


moral:
look at
curves!

$$\text{or } I_D = k (V_{GS} - V_P)^2 \quad \text{or } V_T \quad \textcircled{2} \quad (\text{high } V_{DS})$$

"saturation"


finally, for very small $I_D (< 1\text{mA})$, $I_D = k' e^{V_{GS} - V_P}$ $\textcircled{3}$
and high V_{DS} ,

Simple current source:

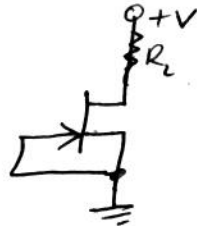

Operate in sat. region. Then
 $I_L = I_{DSS}$, apparently $(= k V_P^2)$
set by device.

To vary, use "self-biasing"

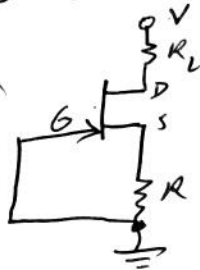

Since $I_G = 0$, quite accurately,

$$V_{GS} = 0 \text{ here } I_S = I_D.$$

$$\text{Also } V_{GS} = -I_S R = -I_D R$$

So we have a $(-)$ bias.

$$\text{Current will be } I_D = k (I_D R - V_P)^2$$

$$(\text{still indep. of } V_{DS}) \quad \text{or } I_D = \frac{1}{KR^2}$$


Transconductance --

Most commonly, amps are ~~def~~ designed

using $g_m \equiv \frac{i_d}{V_{GS}}$ $\leftarrow$ change in drain current.
Measured in "mhos".


It's smaller than for junction transistors

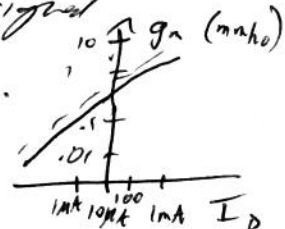$\Rightarrow$ high input Z is main FET virtue.



$$g_m \sim 2\sqrt{kI_D}$$

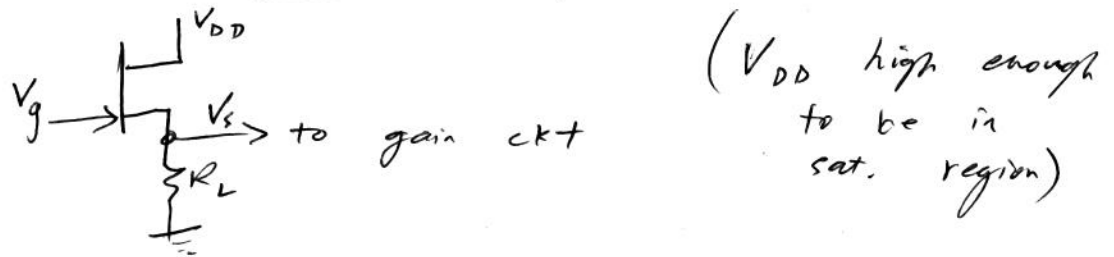One common use is JFET input circuit ---
simplest is source follower --



$$V_s = i_d R_L, \text{ since } I_s = I_D.$$

$$\text{Using } i_d = g_m v_{gs} = g_m (v_g - v_s),$$

$$v_s = \left(\frac{R_L g_m}{1 + R_L g_m} \right) v_g$$

(but note that $g_m \approx 2\sqrt{K I_D}$ depends on operating point!)

$$\approx v_g \text{ if } R_L g_m \gg 1$$

Output impedance is $\frac{1}{g_m}$, like emitter follower, but less impressive ($\sim 100 \Omega$). However, Z_{in} is very large, especially with MOSFETs.

Another common use is variable resistor.

When ① applies -

$$\frac{I_D}{V_{DS}} = \frac{1}{R_{eff}} = 2K \left(\underbrace{(V_{GS} - V_P)}_{\text{linear}} - \frac{V_{DS}}{2} \right)$$

Usable values --- few Ω to ∞ .

Suggest use for: modulators

gain control


→ analog switch

run with this
small, obviously.
(can also compensate
by circuit design -
see H&H.)

But usually we use MOSFET's for this ---


Typical MOSFET:

(NMOS)

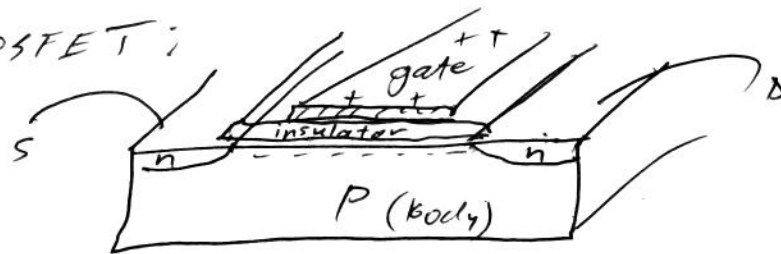

Enhancement mode: make gate (+) to create an n-type channel for conduction.

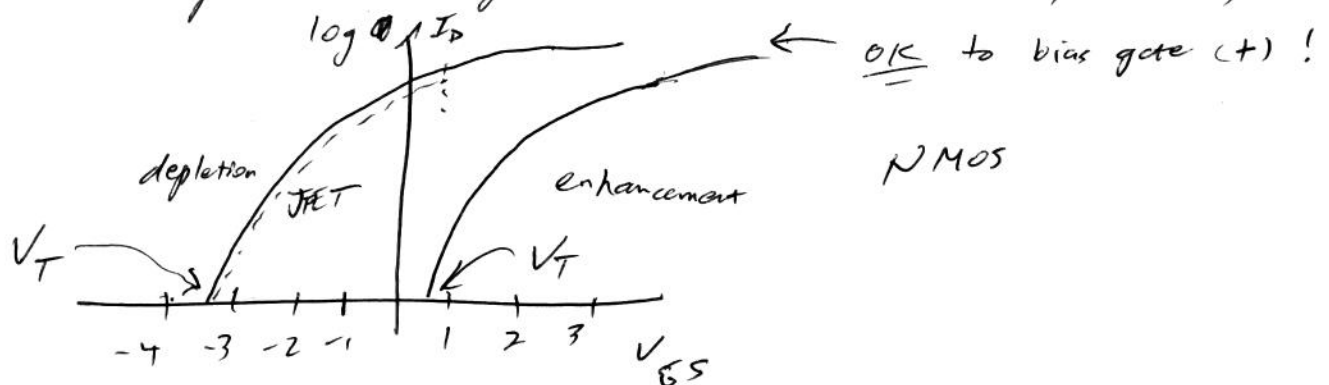Depletion mode: vary doping so a (-) voltage discourages conduction. (fairly rare)



p-channel: mirror image.


So, we usually use MOSFETs as switches.

- no gate leakage (but there is capacitance!)
- 0V is "OFF"

Symbols:




n-channel

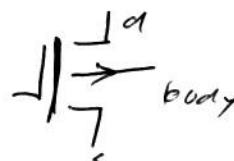

p-channel

body usually connected to S, or ground, in power MOSFETs.

Typical switch -- analog:

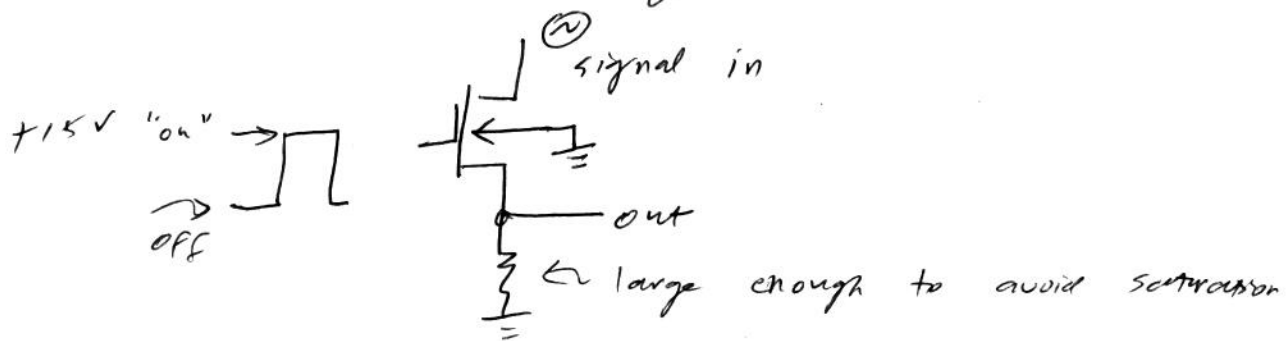


R_{DS} varies from $\sim 10^{10} \Omega$
to $25-100 \Omega$


Can be used for multiplexer, reset, etc.

Nice integrated switches available.

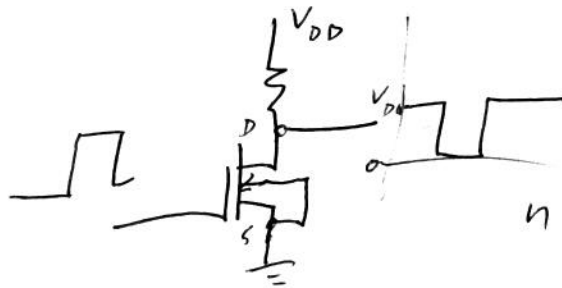logic & power switching: common-source inverter





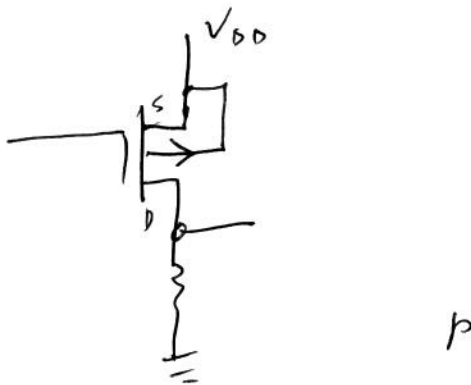For power designs,
can have $R_{on} \approx 0.01 \Omega$!!



Good for driving loads.

Better is

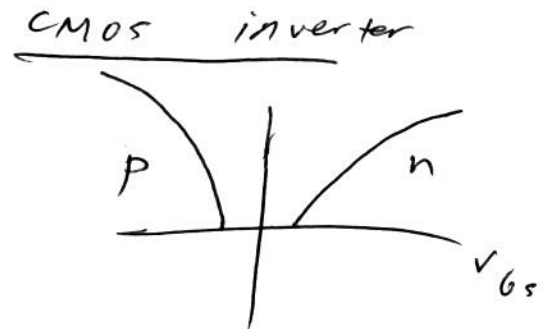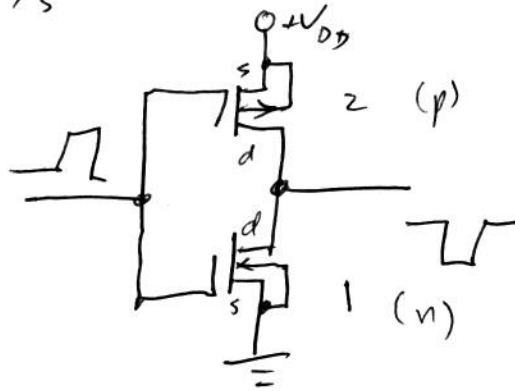

input grounded --- $V_{gs1} = 0$ (off)
 $V_{gs2} = -15V$ (~~off~~ ^{on})

Basis of logic chips

Power FETs -- same with big gates (high C , low R_{on})

- Can have on-state R of $< 0.005 \Omega$
- Currents up to $> 100 A$
- Voltages " " $> 1000 V$
- thermally stable - can use in //.

But,

- 1) Large capacitance -- high gate currents needed to switch rapidly
- 2) Static - sensitive
- 3) Easily damaged by reverse gate bias outside specs.
- 4) Need $\approx 10 V$ to fully switch on, in some cases.
- 5) Body connected to source; forms a diode:

