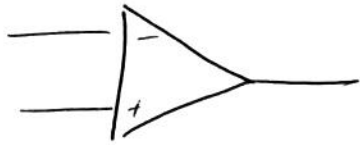


Operational amplifiers


Assume ideal for now

Usual
Version



comp (usually optional or absent)

actual
connections:

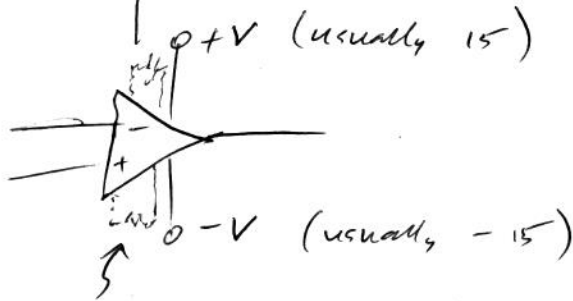

bal. (optional, sometimes absent)


(no ground)

Properties (we will look at real op amps later)

- 1) No input current $(Z_{in} \sim \infty)$ or ΔV_{in}
- 2) output = $((+) - (-)) \times \infty$ $(Z_{out} \sim 0)$


Intended for use with - feedback:

Follower illustrates

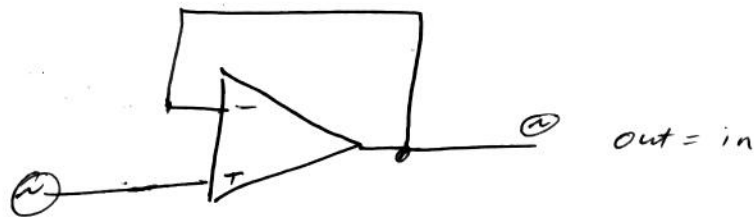

Output will always try to set itself

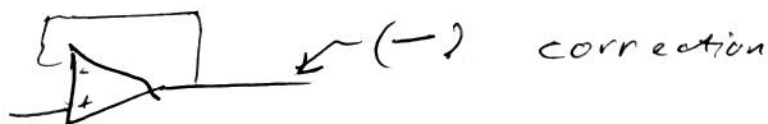so -, + inputs are at same V . To see, assume (+) at 1V, (-) at 1.1V



(In fact, this works even with finite gain,
so long as $Z_{in} = \infty$.)

Compliance range:

Typ. from $\approx -V_{+2}$ to $+V_{-2}$ for older designs


"Special" types go all the way to

One or both supplies, within ~ 10 mV or so.

Now quite common due to battery-powered devices.

Basic amplifiers (dc coupled):

Non-inverting:

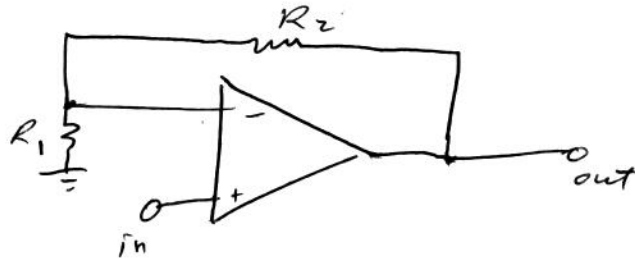

① $V_- = V_{in}$ due to ∞ feedback.

② $V_- = \frac{R_1}{R_1 + R_2} V_{out}$ (exactly, since $I_{opamp} \approx 0$)


$$\text{So } V_{out} = \frac{R_1 + R_2}{R_1} V_{in}$$

$$\boxed{\frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}}$$

$Z_{in} \approx \infty$ (for LF411 $\approx 10^{12} \Omega$)

Z_{out} very low, at least for low freq., small signals.

Inverting

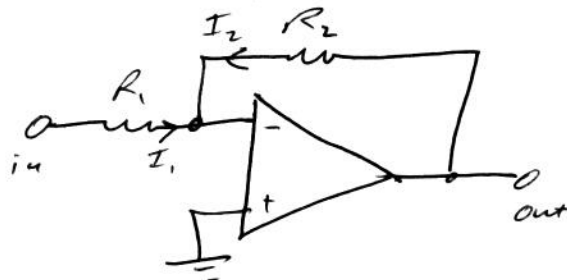


① $V_- = 0$ ② $I_1 = -I_2$ or $V_{in}/R_1 = -V_{out}/R_2$

So gain $\boxed{\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}}$

$$\begin{cases} Z_{in} = R_1 \\ Z_{out} \approx 0 \end{cases}$$


Most common configuration. This is partially because of the "virtual ground" at (-). It lets us build a

Summing amplifier

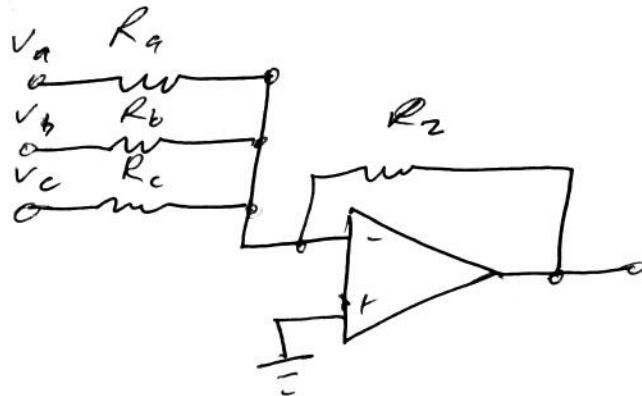

(-) Still at ground, so $I_{tot} = 0 = I_a + I_b + I_c - I_2$
 and $V_{out} = -R_2 \left(\frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} \right)$

(Variant:)

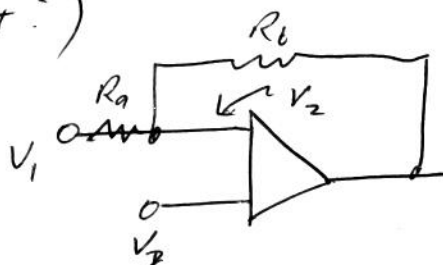


$$(V_1 - V_2)/R_a = -(V_{out} - V_2)/R_b$$

$$\frac{V_{out}}{R_b} = \frac{V_2}{R_b} + \frac{V_2 - V_1}{R_a}$$

$$V_{out} = (V_2 - V_1) \frac{R_b}{R_a} + V_2$$

The variant is a differential amplifier, but a bad one. However, inputs are asymmetric, and ~~input~~ output is not ^{rel.} to ground, but rather to V_2 .

Better differential amplifier ---

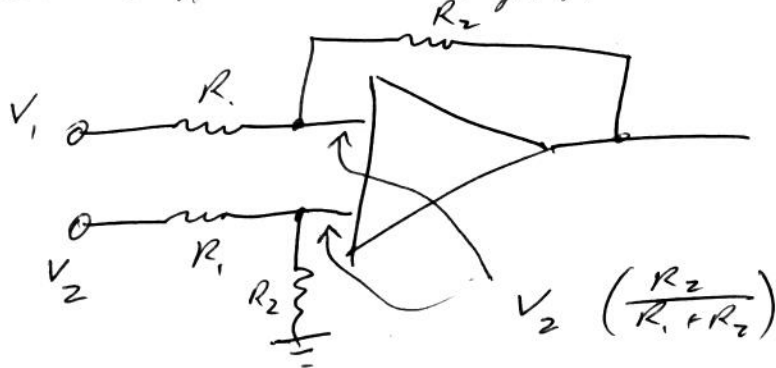


We have
$$\frac{V_1 - V_2 \frac{R_2}{R_1 + R_2}}{R_1} = - \frac{V_{out} - V_2 \frac{R_2}{R_1 + R_2}}{R_2}$$

$$\begin{aligned} \frac{V_{out}}{R_2} &= \frac{V_2}{R_1 + R_2} + \frac{V_2 \frac{R_2}{R_1 + R_2} - V_1}{R_1} \\ &= \frac{V_2 R_1 + V_2 R_2 - V_1 (R_1 + R_2)}{R_1 (R_1 + R_2)} \\ &= \frac{(V_2 - V_1) (R_1 + R_2)}{R_1 (R_1 + R_2)} \end{aligned}$$


$$\boxed{V_{out} = \frac{R_2}{R_1} (V_2 - V_1)}$$

But, need precisely matched resistors!

Problem is common-mode rejection ---

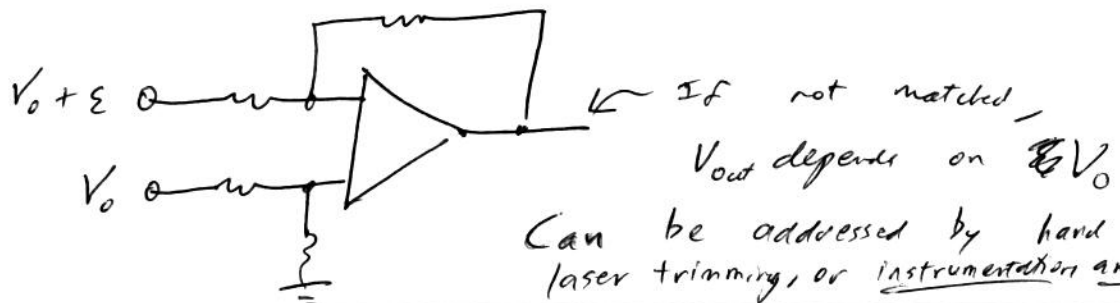


Linearized power amplifier ---

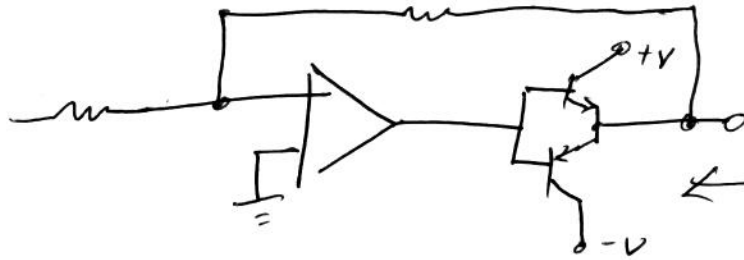

(In practice, add
• protection
• bias
• thermal stabilization)

Can do same with HV output:

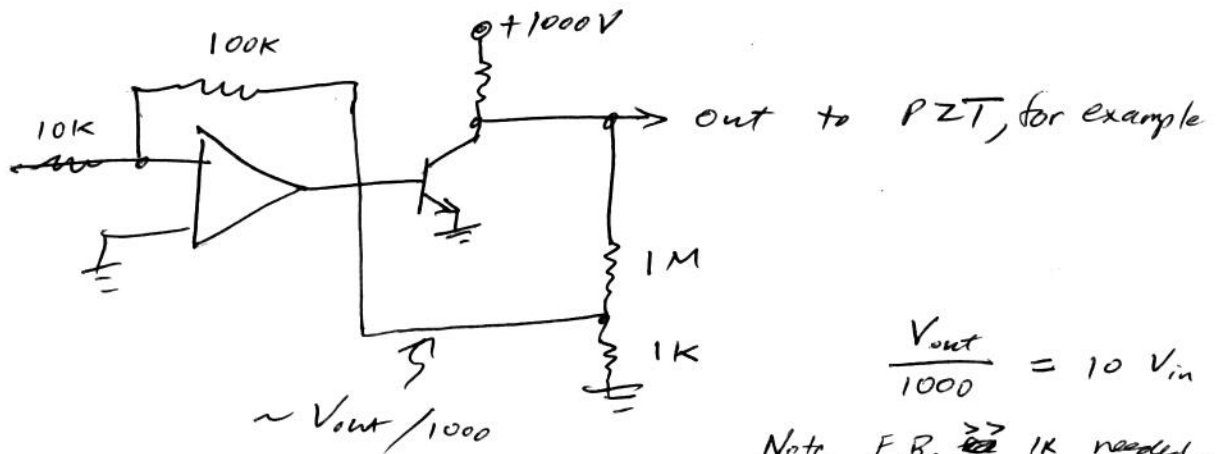


$$\frac{V_{out}}{1000} = 10 V_{in}$$

Note F.B. ~~1K~~ 1K needed.

Even better: use single-chip solutions such as -

- 1) Texas Instruments OPA548T: up to 60V, up to 3A, ~\$15.
- 2) Apex/Cirrus PA340CC: up to 350V, up to 0.12A, ~\$25.

Transimpedance amplifier:

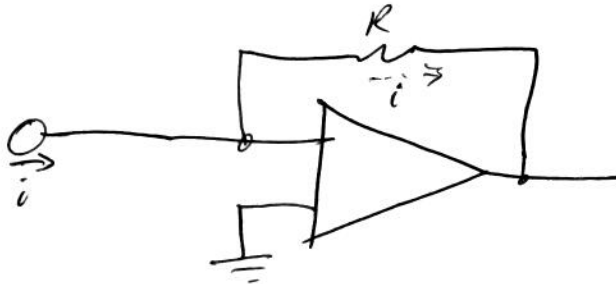


$$V_{out} = -R i_{in}$$

$$Z_{in} = ? \quad (o)$$

This is used with photodiodes and similar detectors



$I \propto$ photon flux
(eff; about 50%)

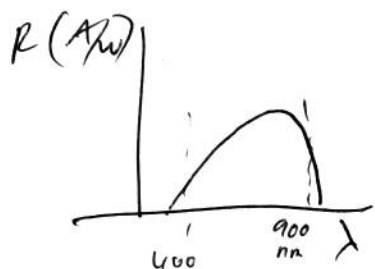

At 633 nm, $E = h\nu = h \frac{c}{\lambda}$

$$= (6.63 \times 10^{-34} \text{ J}\cdot\text{s}) \frac{3 \times 10^8 \frac{\text{m}}{\text{s}}}{633 \times 10^{-9} \text{ m}}$$


$$= 3.14 \times 10^{-19} \text{ J}$$

$0.1 \text{ mW} \Rightarrow 3.2 \times 10^{-4} \text{ J/s}$, or $3.2 \times 10^{14} \text{ J/s}$



Current $I_p = 0.5 \times \left(\frac{3.2 \times 10^{-4} \text{ J/s}}{3.14 \times 10^{-19} \text{ J}} \right) (1.6 \times 10^{-19} \frac{\text{C}}{\text{e}})$

$$= 26 \mu\text{A} \quad \text{or} \quad 0.26 \frac{\text{A}}{\text{W}}$$

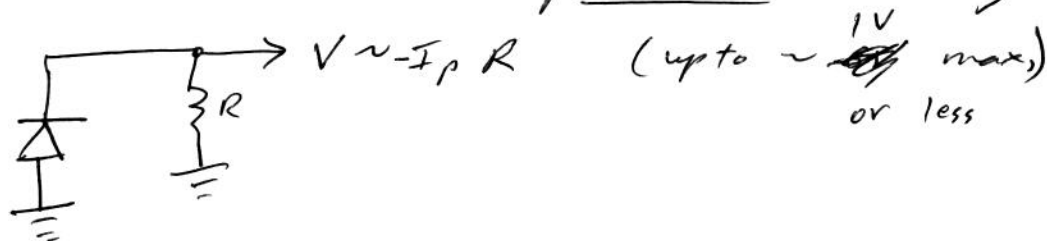Sometimes used instead in photovoltaic mode,



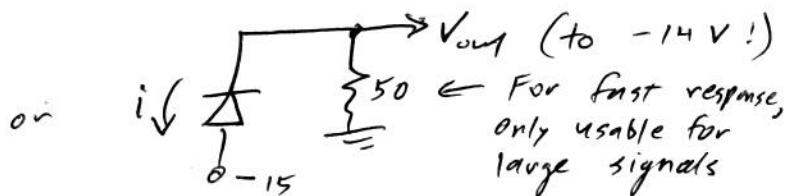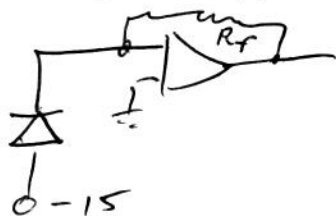Often used with reverse bias, to reduce capacitance:



The op amp helps to minimize effects of stray C_s too.

Since $Z_{in} \approx 0$, the time constant RC does not apply.


Instead, a detailed analysis shows that

$$f_{3dB} \approx \sqrt{\frac{f_T}{2\pi C_{diode} R_F}}, \quad f_T = \text{unity-gain frequency or "gain-bandwidth product".}$$

For a perfect op amp, there would be no limit!

Arbitrary feedback:

OPA-7

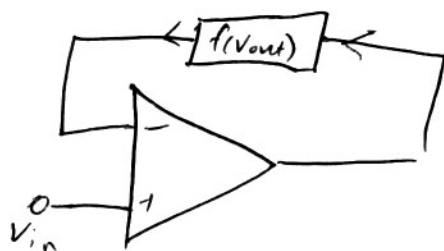

$$f(V_{out}) = V_{in}$$

$$\text{So } V_{out} = f^{-1}(V_{in})$$

Can also do with (-) in, if device in loop produces a current rather than a voltage output:



$$\frac{V_{in}}{R} = -g(V_{out})$$

$$V_{out} = -g^{-1}\left(\frac{V_{in}}{R}\right)$$

So if $g = e^V$, $V_{out} = -\ln \frac{V_{in}}{R}$ (see H&H for such a circuit)

Ex: integrator




$$\frac{V_{in}}{R} = -C \frac{dV_{out}}{dt}$$
$$V_{out} = -\frac{1}{R} \int_0^t V_{in} dt + V_{initial}$$

This is exact! The virtual ground keeps it that way.


(But in real op amps, also get $\int V_{offset}$)

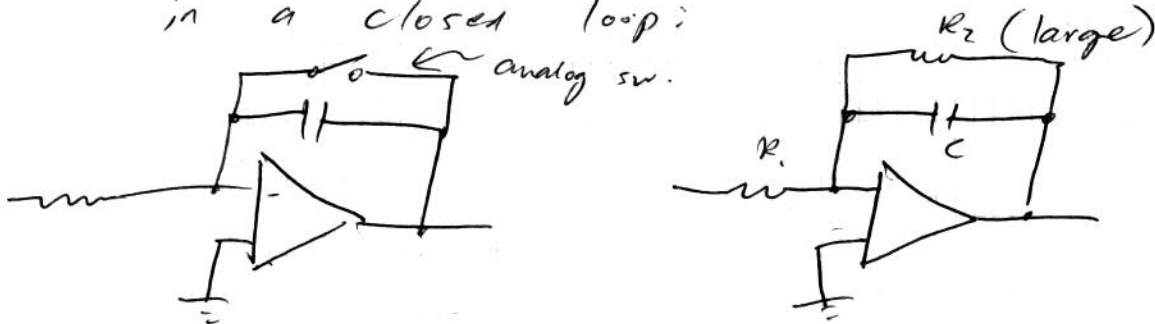Integrator needs a reset, or a resistor to set a finite dc gain, unless in a closed loop:




High freq: $-\frac{1}{R_i C} \int V_{in} dt$

Low freq: $-\frac{R_2}{R_i}$

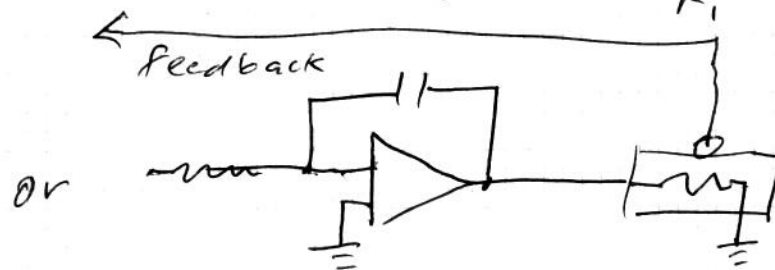

(gives a gain, in effect) often summed w/ linear gain.

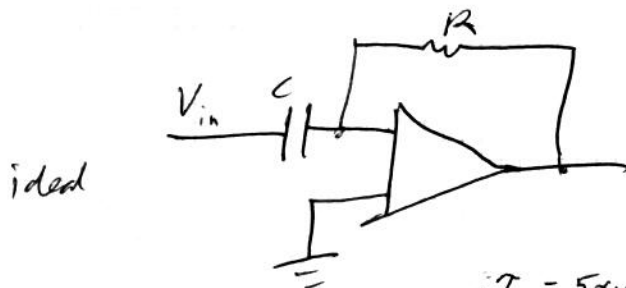Differentiator: same basic theme, but C not in feedback:




ideal

$$C \frac{dV_{in}}{dt} = - \frac{V_{out}}{R}$$

$$V_{out} = -RC \frac{dV_{in}}{dt}$$


actual (stable)

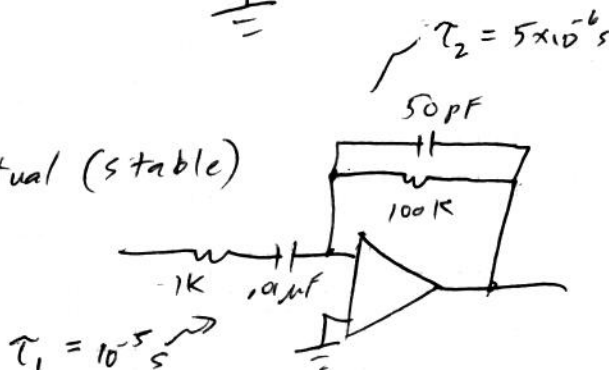


$\tau_1 = 10^{-5} s$

integrator for large ω

Filters

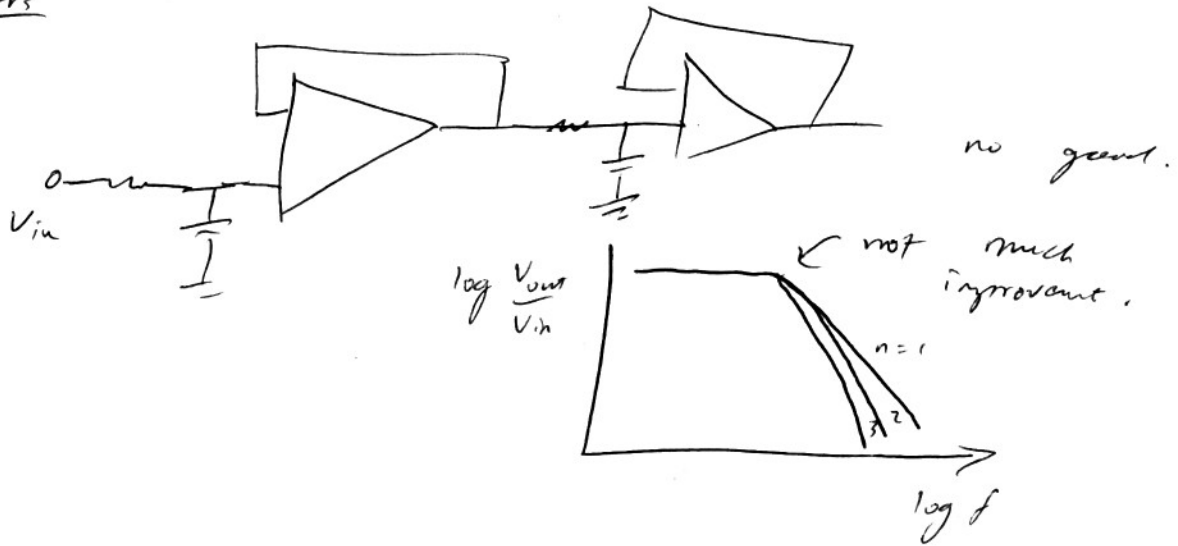


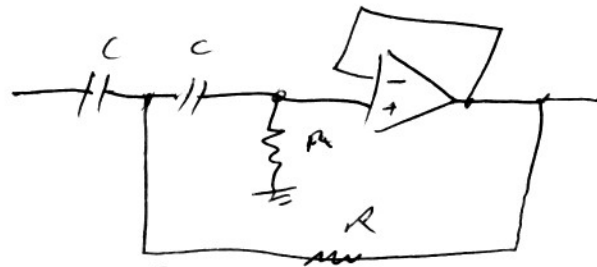Instead, multi-pole active filters are used ;
can synthesize only RLC Filter without loading prob's!




Basic Sallen & Key filter

"Bootstrapping" sharpens rise

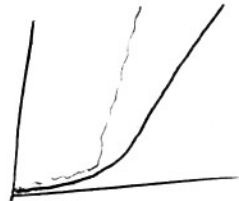

Oscillators -- classic cheap example is
a 555 timer chip --- uses positive feedback.

Simplest is relaxation osc ---

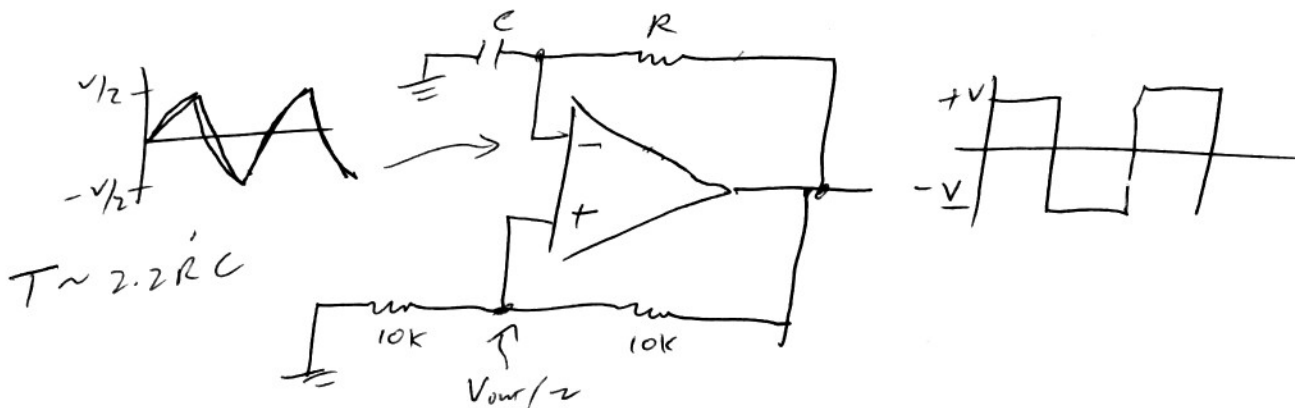



Real op Amps I

ac op amp behavior



OPA-10

Finite gain; instability.

Recall the behavior of an RC low-pass:

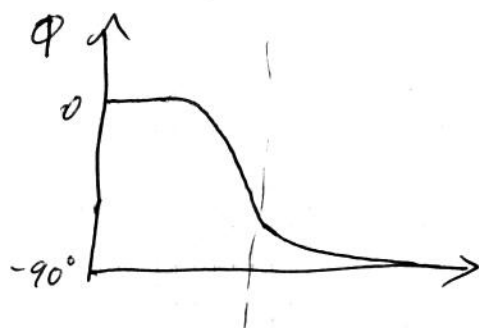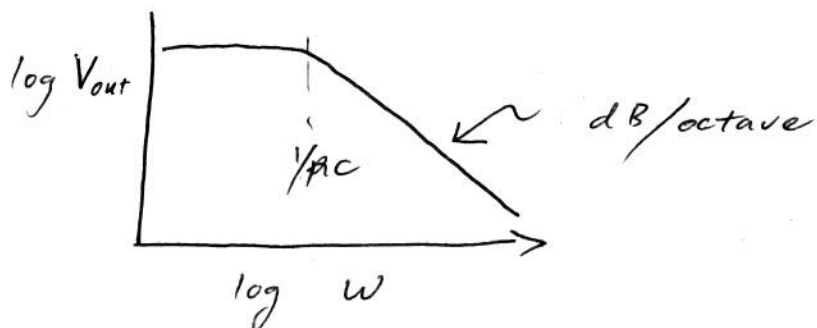

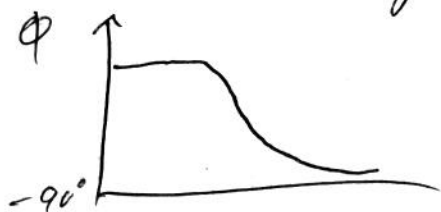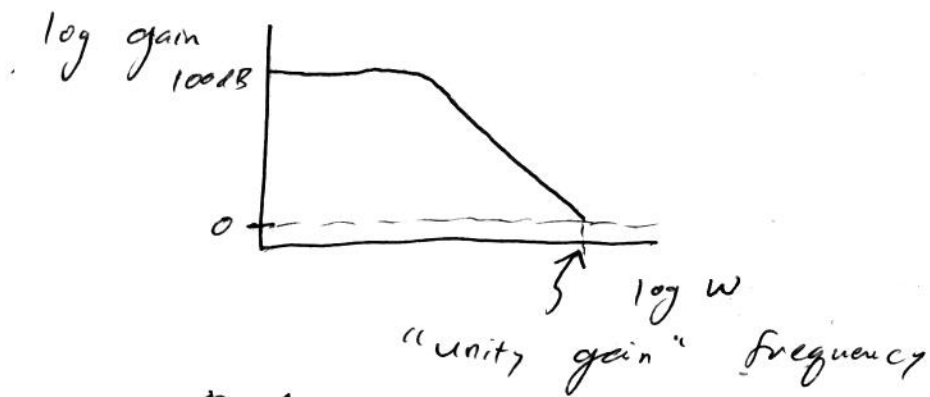Most op-amps have a dominant "pole" so they look very similar ---




($\times (-1)$ if inverting)

- Causes loss of accuracy
But what if we have additional phase lag?

If $|\phi| > 180^\circ$, neg. feedback $\rightarrow$ positive. So we get instability, and excursions at ω will be amplified $\rightarrow$ oscillation!

Look at these problems in turn:

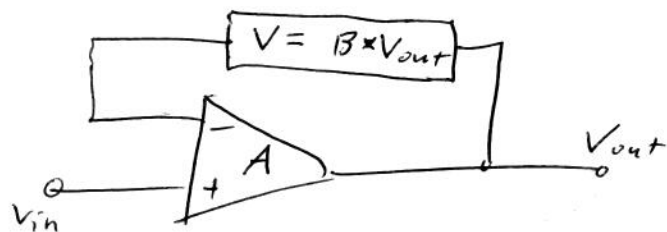- 1) Finite gain. As an example, look at a non-inverting voltage amp (other configs. are similar):




If $A = \infty$, $G = \frac{1}{B}$ ($V_{out} = \frac{1}{B} V_{in}$)

But now, $V_{out} = A (V_+ - V_-)$
 $= A (V_{in} - B V_{out})$

$$V_{out} = \left(\frac{A}{1 + AB} \right) V_{in} \quad (1)$$

← G

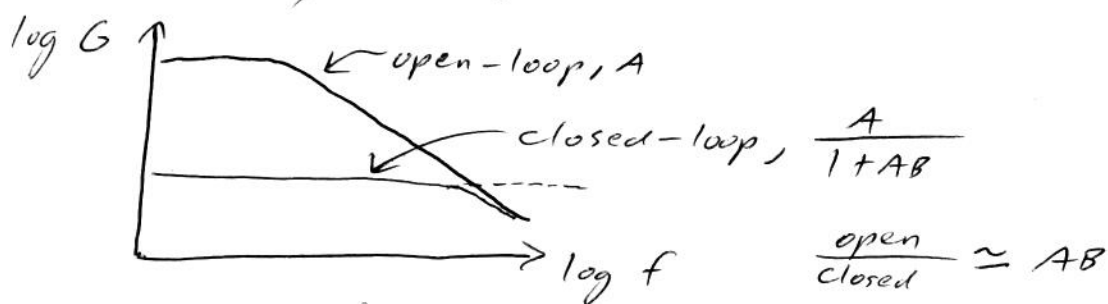So, if we have a "single-pole" frequency rolloff, 6 dB/octave,



So, (a) Finite gain changes G

(b) Frequency response is limited by gain rolloff.

Also, both Z_{in} and Z_{out} are ~~diminished~~ affected

IF we have for open-loop,



Then for closed loop,


$$I_{in} = \frac{V_{in} - B V_{out}}{R_{in}} = \frac{V_{in}}{R_{in}} \left(1 - \frac{AB}{1+AB} \right) = \frac{V_{in}}{R_{in} (1+AB)}$$

Thus $Z_{in} = \frac{V_{in}}{I_{in}} = (1+AB) R_i$ (not 0)

Likewise, can show $Z_{out} = \frac{1}{1+AB} R_o$ (not zero)
 ← open-loop output imp.

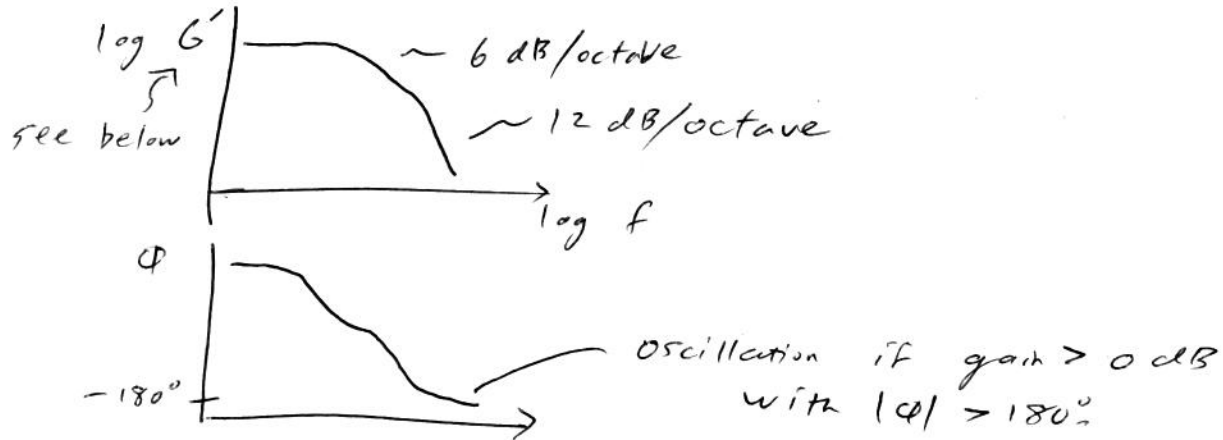2) Stability (a major issue in real designs)



If there happen to be two poles, due to external components,



Assuming load/feedback are well-behaved, worst case is unity gain, because what counts here is the loop gain AB , which determines how much is fed back. (It's also $\approx \frac{\text{open-loop gain}}{\text{closed-loop gain}}$.)

Compensation is used to assure stability.

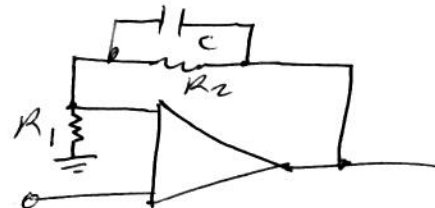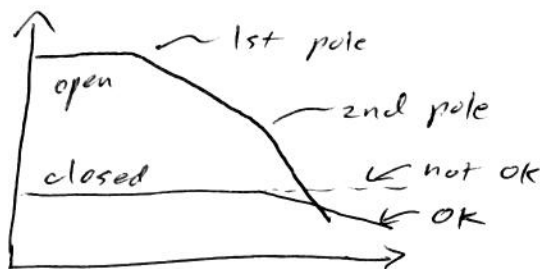Basic idea: make sure that closed-loop gain for $A = \infty$ intersects open-loop gain with slope $\ll 12 \text{ dB/octave}$.




$$B = \frac{R_1}{R_2 // \frac{1}{i\omega C} (+R_1)}$$

Differentiator obviously horrible, needs lots of work to assure stability.

The 411, like the 741, is already unity-gain compensated internally.


Note: poles, zeroes refer to response function, & Laplace transform language.

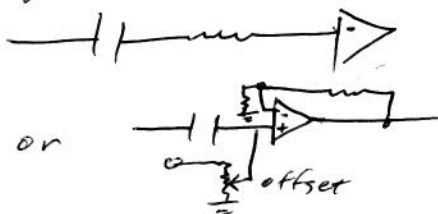ac coupling: use when appropriate to eliminate offsets




Real Op Amps II - Basic physical limitations

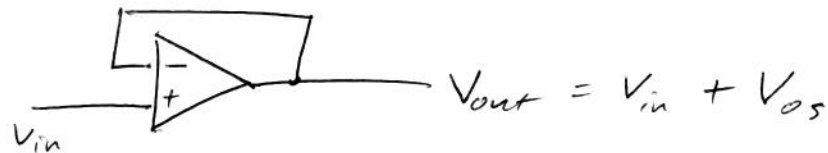- 1) Input offset voltage: V_- held at $V_+ - V_{os}$, not V_+ .
In a follower, replicated at output;




In amplifiers, can be amplified

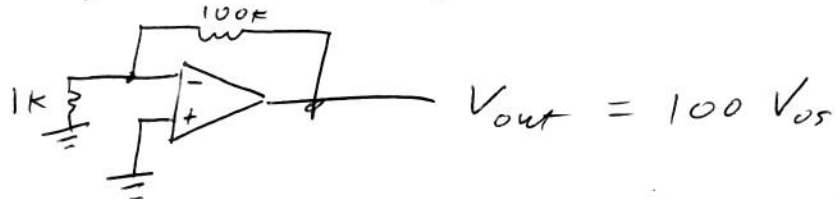

LF411: 0.8 mV typ., $7 \mu\text{V}/^\circ\text{C}$
741: 2 mV, $\sim 10 \mu\text{V}/^\circ\text{C}$ $\swarrow$ has trimming provisions.
AD8551: 0.001 mV, $0.005 \mu\text{V}/^\circ\text{C}$

- 2) Offset & bias current

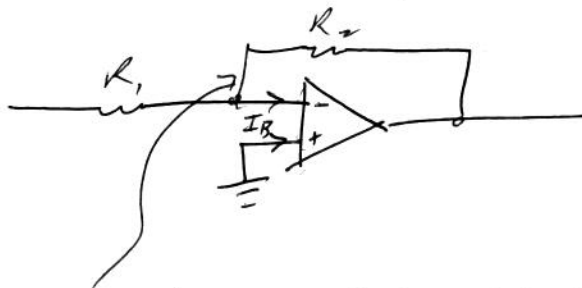

$$|I_-| \approx |I_+| = \text{bias current}$$

Ignoring V_{os} , $V_- = \Delta V_- = I_B (R_1 \parallel R_2)$ rel. to perfect op amp.

$$\Delta V_{out} = -\frac{R_2}{R_1} \Delta V_-$$

$$\approx R_2 I_B \text{ if } R_2 \gg R_1$$

741: 500 nA

LF411: 0.2 nA

AD549L: 60 fA (!) not pA!


Can often be compensated:



741: 200 nA
LF411: 0.1 nA

However, there's still the input offset current $I_{os} \equiv I_+ - I_-$.
For many modern op amps, not that much smaller than I_{bias} .
For ac signals, ac coupling eliminates.

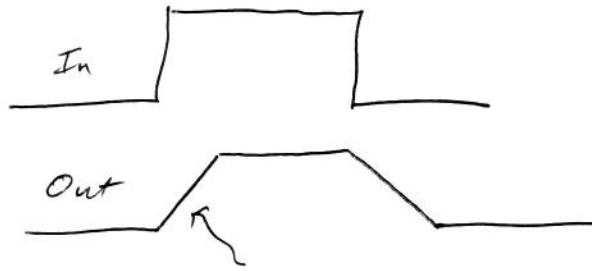3) Slew rate = response to large-signal step function



Determined by current limitations of output stages.
 $\neq$ bandwidth

741: $0.5 \text{ V}/\mu\text{s}$

LF411: $15 \text{ V}/\mu\text{s}$

LF311: $\sim 25 \text{ V}/\mu\text{s}$ (with 500Ω pulling to ± 5)

AD8009: $3500 \text{ V}/\mu\text{s}$

4) Output swing: "rail to rail" op amps can drive to $< 20 \text{ mV}$ wrt supply voltages --- some run off a single 1.5 V battery.


5) Common mode rejection -- typ. $> 100 \text{ dB}$, usually limited by external circuitry.

6) Finite gain and phase shifts $\Phi(\omega)$ — to be discussed shortly

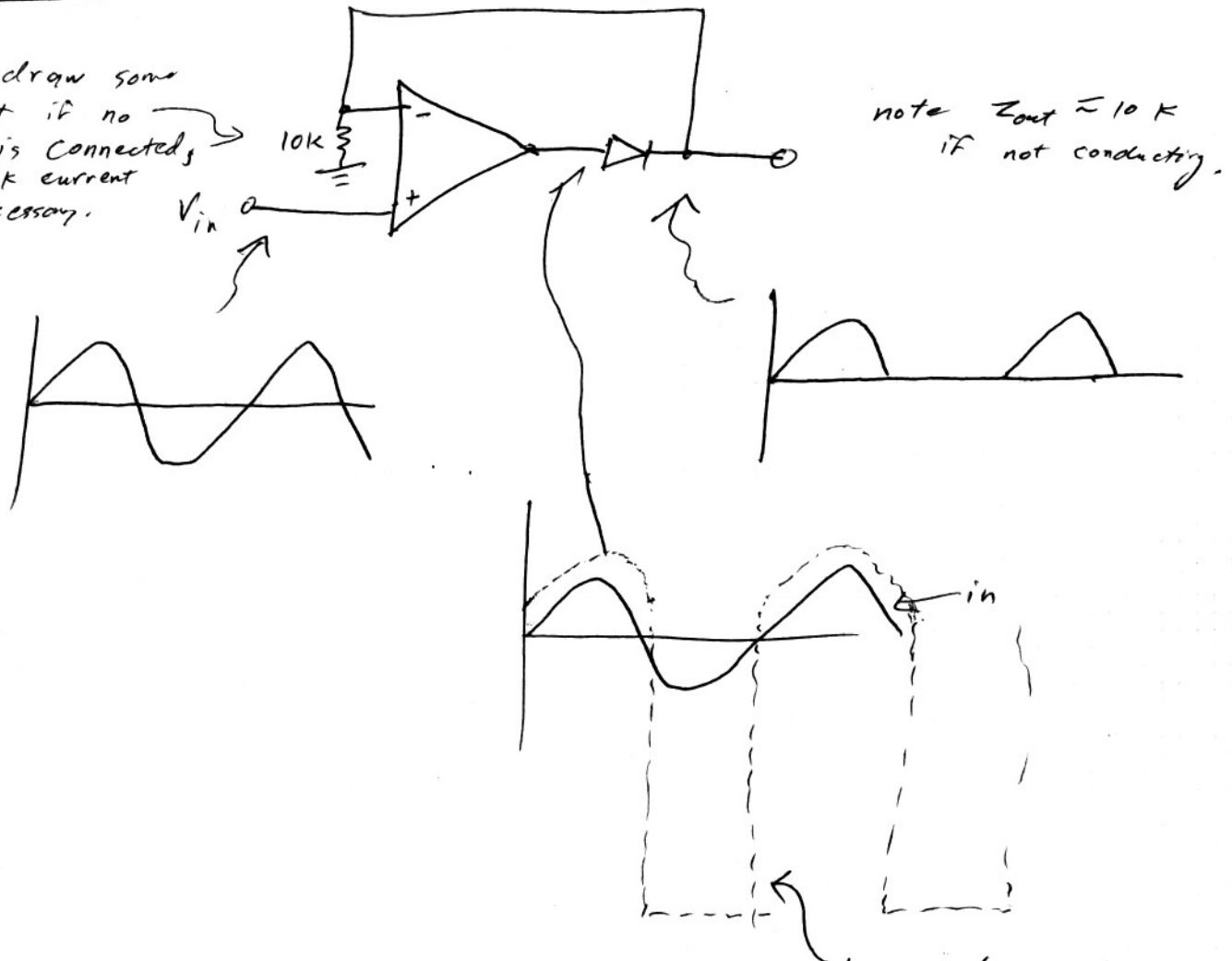7) Noise: 1. low-frequency
 2. white noise ($\text{nV}/\sqrt{\text{Hz}}$) } Will discuss later.

"Superdiode"


to draw some current if no load is connected, or sink current if necessary.



note $Z_{out} \approx 10k$ if not conducting.

Full-wave variations (see H&H) can be used for measuring $\bar{V}$, etc., or for calculating $|V_{in}|$

Improved:

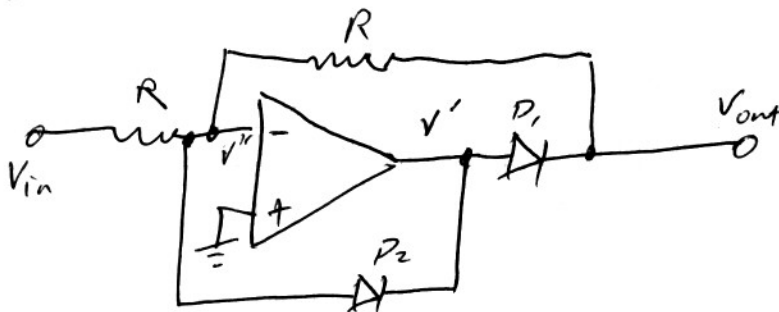

(-) in $\Rightarrow D_1$ conducts, gain -1

(+) in $\Rightarrow D_1$ reverse-biased


D_2 clamps V' at $-0.6V$ so $V''=0$.

Here $V_{out} = 0V$, but impedance $\sim R$. $\Rightarrow$ use follower if needed.

Comparators

OPA-16

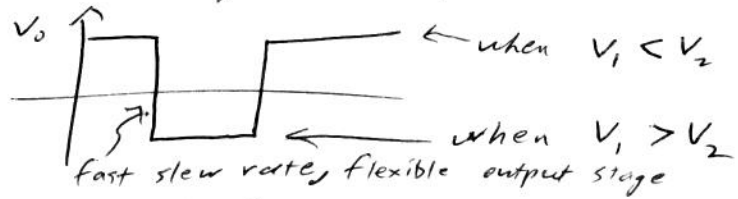They are really just op amp - like devices meant to operate without feedback, or even with (+) feedback. Typically they switch very quickly and cleanly between two output states.




LM311 is a classic comparator (open collector output needs pullup)

A Schmitt trigger is often used to detect logic transitions on a noisy signal line:



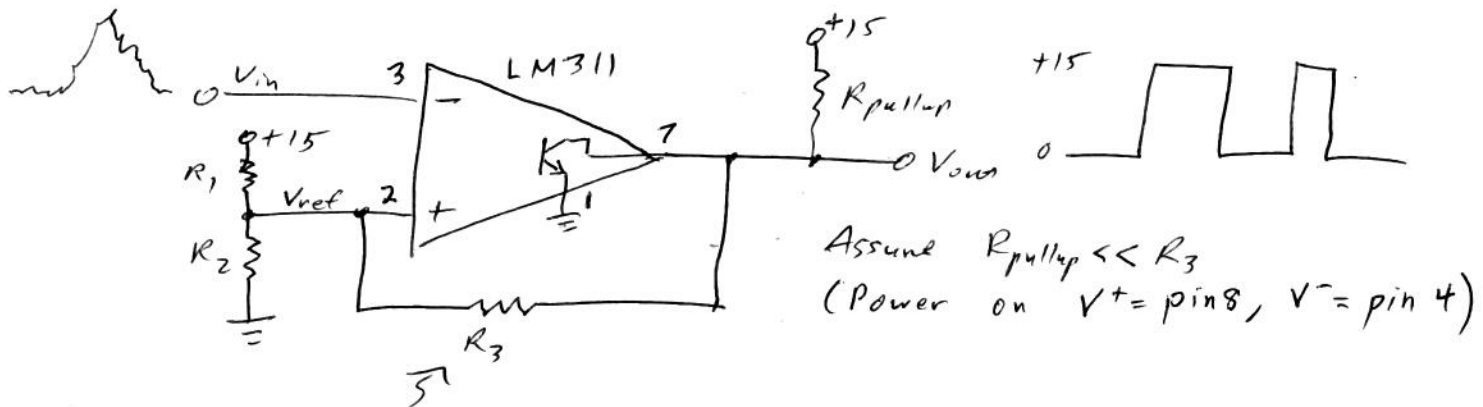Often built into line receivers. Can be manually set using a comparator and resistors — for example,



Parallels R_2 if output at 0V, so

$$V_{ref} = V_{LO} = \frac{R_2'}{R_1 + R_2'} (15V), \quad R_2' = R_2 // R_3$$


Parallels R_1 if output at 15V, so

$$V_{HI} = \frac{R_2}{R_1' + R_2} (15V), \quad R_1' = R_1 // R_3$$

and if R_3 is fairly large, $V_{HI} > V_{LO}$

If hysteresis small, R_1, R_2 sets threshold, $R_3' (R_1 // R_2)$ sets fractional hysteresis.

Typ. Control system:

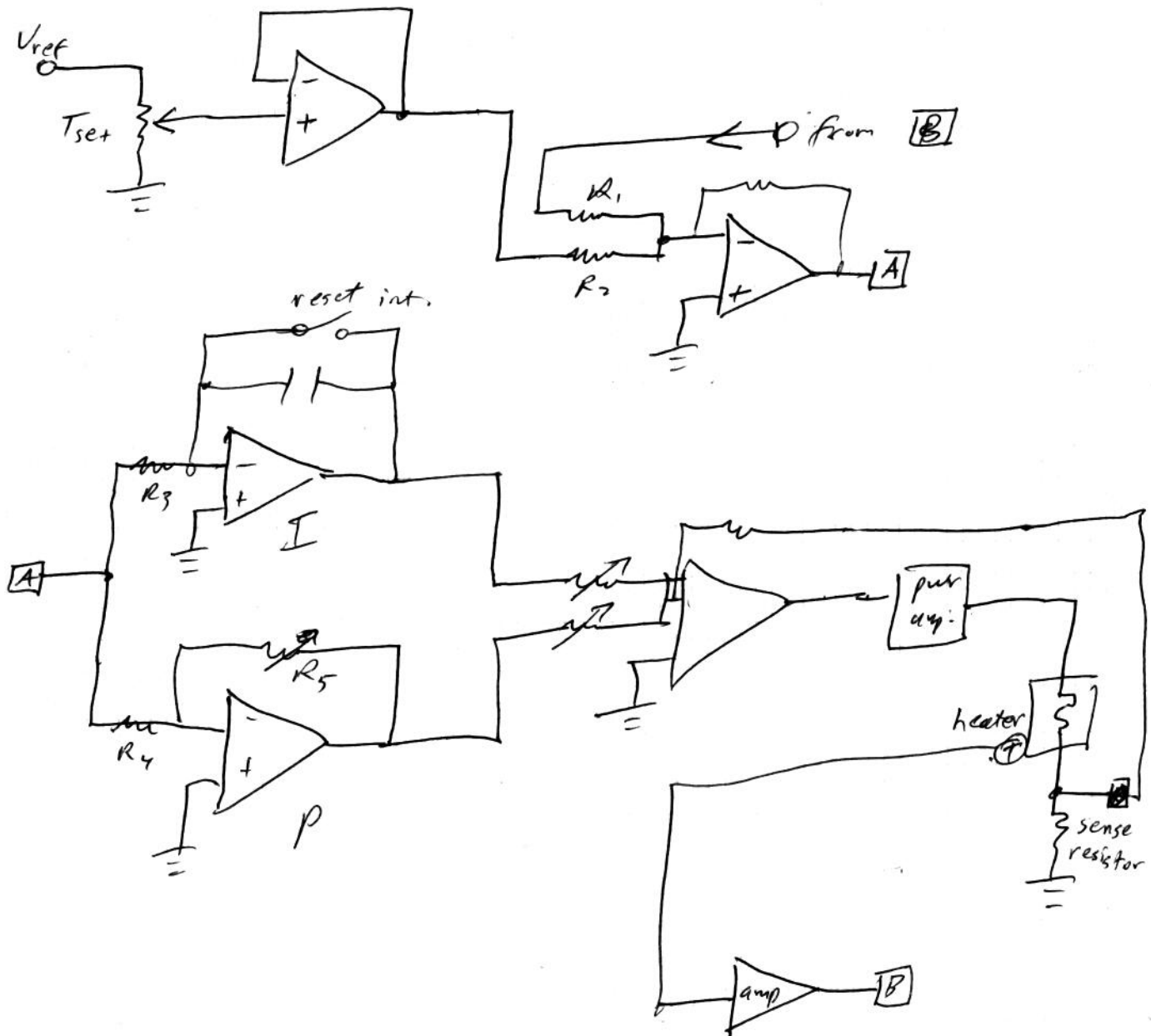

- Sometimes a differentiator is added — "PID" controller
- Why are buffers used?
- Why is integrator there?
- probably not stable as shown!
- In practice, usually use a thermistor + voltage source for (T), and an instrumentation amp.