

Capacitors and Inductors -- ac Circuits

↙
store electric field

↖ store magnetic field

Basic equation of a capacitor is

$$\frac{1}{\text{---}} C$$

$$Q = C V$$

↙ constant capacitance, in Farads (F)
(most often pF or μF .)

Using $I = \frac{dQ}{dt}$, we can write eqn's for behavior of capacitive circuits.

For an inductor,

$$\text{---} L$$

$$V = L \frac{dI}{dt}$$

So one depends on $\frac{dI}{dt} = \frac{d^2Q}{dt^2}$, the other on $Q = \int I dt$.

Signs: for C, - if moving from +Q to -Q ---

$$\Delta V = -\frac{Q}{C} \quad (-) \quad \left\{ \begin{array}{l} \text{---} V_0 + V \\ \text{---} V_0 \end{array} \right.$$

(much like resistor)

for L, $-L \frac{dI}{dt}$ in direction of I.

Types:

1) Mylar ---




just roll up!

general purpose

2) ceramic -- dielectric is a ceramic

(good at rf)

3) electrolytic

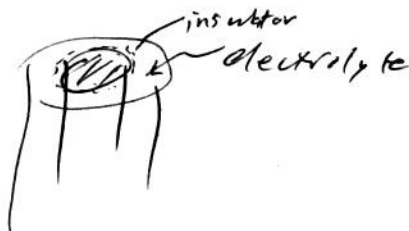

(+), (-) vital!

leaky, but high C for size.

4) Metallized plastics (polyester, etc.)

Biggest trick -- reading values!

Usually, in either pF or μF . (If in doubt, use a DMM with capacitance ranges)



M means $\pm 20\%$

Voltage rating may or may not be stamped.

Use common sense


Sometimes coded like precision resistors; exponential labeling --
575 means 57×10^5 pF, or $5.7 \mu\text{F}$

Analysis of RC circuits:

Three approaches

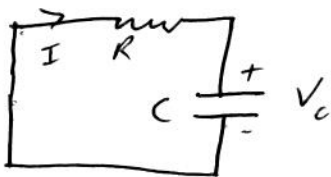- 1) Direct solution (easiest for impulse response).
- 2) Response to sinusoidal excitation --- Impedance
- 3) (later) Laplace x-forms (s-space)

Basic RC circuit (without driving --- transient sol'n)



Assume $V_c = V_0$ at $t=0$

loop theorem:

$$-IR - V_c = 0$$

$$V_c = \frac{Q}{C} = -IR$$

$$\frac{dQ}{dt} = -RC \frac{dI}{dt}$$

$$\text{or } \frac{dI}{dt} = -\frac{1}{RC} I$$


$$\text{Sol'n: } I = I_0 e^{-t/RC}$$

or since $I = C \frac{dV_c}{dt}$, or ~~better~~ easier, $V_c = IR$,


$$\boxed{V = V_0 e^{-t/RC}}$$

where $V_0 = I_0 R$ at $t=0$

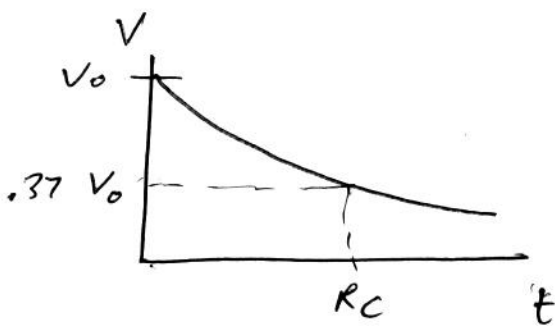(will be zero unless circuit looked different before $t=0$.)



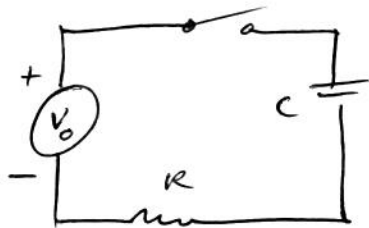This is a discharge cycle; charging is quite analogous:



$$V_0 - V_c - IR = 0$$


$$V_0 - \frac{Q}{C} - IR = 0$$

$$-\frac{1}{RC} I = \frac{dI}{dt} \text{ again.}$$

But now $V_c = V_0 - IR$

$$\text{So } V_c = V_0 - I_0 R e^{-t/RC}$$

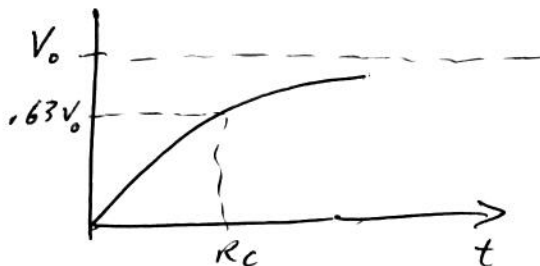
If $V_c = 0$ at $t=0$, $V_c = V_0 (1 - e^{-t/RC})$




just upside down.

In general, relaxes to the state where $I=0$ with time constant RC .

For a slow square wave we see,

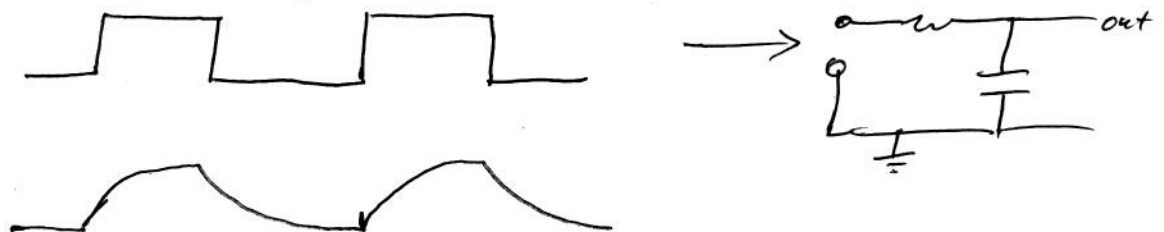


For a fast square wave, $T \ll RC$,

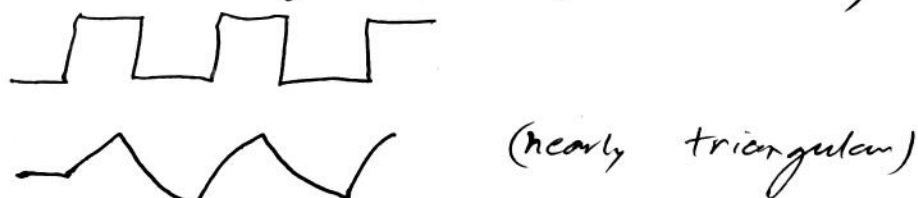

(nearly triangular)

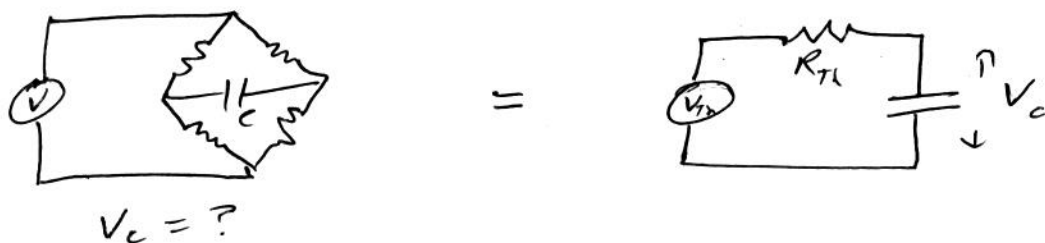For more complex RC's can sometimes use
Thevenin equivalent; makes life a lot easier!



(Actually, we'll see theorem even works for L's & C's
in the part we simplify out!)

So far we have a slow-down circuit.

Alternative interpretation:

Can also use it as an integrator:



$$V_{in} - IR - V_c = 0$$

Write in terms of V_c this time -

$$I = C \frac{dV_c}{dt} = \frac{V_{in} - V_c}{R}$$

If we make RC large, then $V_c \ll V_{in}$ and
for small times

$$\frac{dV_c}{dt} \approx \frac{V_{in}}{RC}$$

$$\text{and } \boxed{V_c \approx \frac{1}{RC} \int V_{in}} (+ V_0), \text{ if } T \ll RC.$$

This is especially effective with op-amps, where
we eliminate the unwanted term altogether!

For square wave, the error is the curvature:



approx. (1st term in Taylor
expn is what's wanted.)

If we look at V_R instead we can form a high-pass or differentiator ---





$$I = \frac{V}{R} = C \frac{dV_C}{dt}$$


$$V_{in} - V_C - V = 0 \Rightarrow \frac{V}{R} = C \frac{d}{dt} (V_{in} - V)$$

For small RC we can get $V \gg RC \frac{dV}{dt}$, and

$$V \approx RC \frac{dV_{in}}{dt}$$

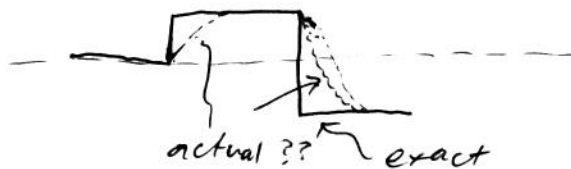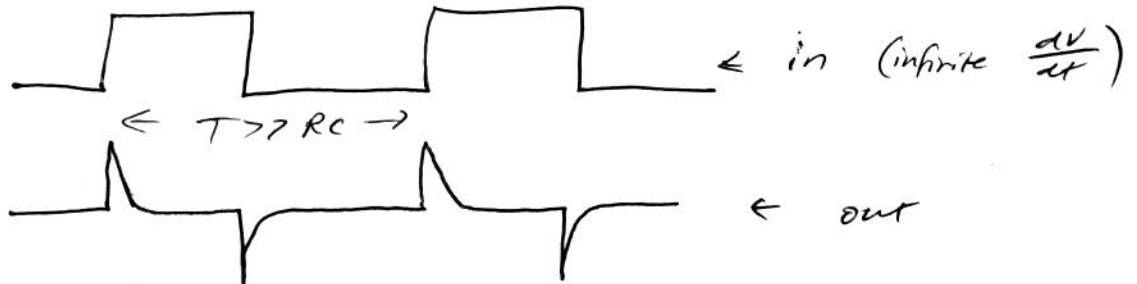

Response to sinusoidal excitation:

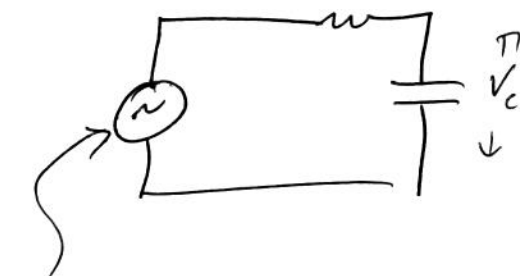

(general, using
Fourier's theorem)

We want the steady-state
solution for V_C .

$$V_{in} = V_0 \cos \omega t$$

$$V_0 = \text{amplitude}$$

$$V_{rms} = \frac{V_0}{\sqrt{2}} = \text{root-mean-square value.} = \frac{V_{p-p}}{2\sqrt{2}}$$

Reason: in a resistor $P = I^2 R$ or V^2/R

$$\langle P \rangle_{\text{cycle}} = \frac{V_0^2}{R} \langle \cos^2 \omega t \rangle = \frac{1}{2} \frac{V_0^2}{R}$$

$$= \frac{V_{\text{rms}}^2}{R}$$

$$V_{\text{rms}} = \sqrt{\langle V(t)^2 \rangle_{\text{cycle}}}$$

So "117 V" (or 120) refers to rms value:
 $\nwarrow$ mean square
 $\nwarrow$ root

$$\left\{ \begin{array}{l} V_0 = \text{amplitude} \\ 2V_0 = P-P \end{array} \right.$$

$$\left\{ \begin{array}{l} \frac{V_0}{\sqrt{2}} = \text{rms value} \end{array} \right.$$

For a sine wave;
 different for other shapes.

Return to our driven circuit now:

$$V_0 \cos \omega t - IR - V_C = 0$$

$$\text{with } I = C \frac{dV_C}{dt},$$

$$\boxed{V_0 \cos \omega t - RC \frac{dV_C}{dt} - V_C = 0}$$

Optional -
 Review of
 Complex Numbers

The idea is to make a guess in complex form,

normally not
 written out

$$\hat{V}_C = \hat{V}_{C0} e^{i\hat{\omega}t}$$

where

$$\text{complex amplitude } \hat{V}_{C0} = A e^{i\phi}$$

gives amplitude & phase

$$\hat{\omega} = \omega' + i\gamma$$

gives freq. & damping
 not needed here!

and where the physical solution is $V_C = \text{Re}(\hat{V}_C)$

Proceed in detail: re-write as

$$\text{Re}(V_0 e^{i\omega t}) - RC \frac{d(\text{Re} \hat{V}_C)}{dt} - \text{Re} \hat{V}_C = 0$$

$$\text{can easily show } \frac{d}{dt} (\text{Re} e^{i\hat{\omega}t}) = \text{Re} \left(\frac{d}{dt} e^{i\hat{\omega}t} \right)$$

$$\text{So } \text{Re} \left(V_0 e^{i\omega t} - RC \frac{d\hat{V}_C}{dt} - \hat{V}_C \right) = 0$$

if $\hat{\omega} = \omega$,
 for driven response,

$$\text{Re} \left[\underbrace{(V_0 - i\omega RC \hat{V}_{C0} - \hat{V}_{C0}) e^{i\omega t}}_{\text{must be 0}} \right] = 0$$

$$\text{So } \hat{V}_{co} = V_0 \frac{1}{1 + i\omega RC}, \quad V_c = \text{Re}(\hat{V}_{co} e^{i\omega t})$$

Looks like a voltage divider if we say that a capacitor has an impedance $Z_c = \frac{1}{i\omega C}$:

$$\hat{V}_{co} = V_0 \frac{Z_c}{R + Z_c}$$



To get phase explicitly, write $|\hat{V}_{co}| e^{i\phi}$

$$\hat{V}_{co} = V_0 \frac{1 - i\omega RC}{1 + (\omega RC)^2} \quad \text{gives } \phi = \tan^{-1}(-\omega RC)$$

$$|\hat{V}_{co}| = \sqrt{\hat{V}_{co} \hat{V}_{co}^*} = \sqrt{\frac{1}{1 + \omega^2 R^2 C^2}}$$

$$\text{and } V_{co} = V_0 \sqrt{\frac{1}{\omega^2 R^2 C^2 + 1}} \cos(\omega t + \phi)$$

$$= V_0 \text{ for } \omega = 0 \text{ since } \phi(\omega=0) = 0$$

Impedance: In general we define at frequency ω ,

$$\boxed{\text{impedance } Z = \frac{\hat{V}}{\hat{I}}} \quad \begin{matrix} \leftarrow \text{Complex amplitudes of} \\ \leftarrow V, I: \end{matrix}$$

$$V = \text{Re}(\hat{V} e^{i\omega t})$$

$$I = \text{Re}(\hat{I} e^{i\omega t})$$

$$\boxed{\begin{array}{ll} \text{Capacitor:} & Z = \frac{1}{i\omega C} \\ \text{Inductor:} & Z = i\omega L \\ \text{Resistor:} & Z = R \end{array}}$$

For a pure capacitor, verify that $Z = \frac{1}{i\omega C}$ works:



$$\hat{V}_0 = \hat{V}_c, \quad \text{obviously}$$

$$= \hat{Z}_c \hat{I}_c$$

$$= \frac{1}{i\omega C} \hat{I}_c$$


In other words, $V = V_0 \cos \omega t$ (this is given)

and $I = \text{Re} (i \omega C V_0 e^{i \omega t})$

$I = -\omega C V_0 \sin \omega t$ (since $e^{i \omega t} = \cos \omega t + i \sin \omega t$)

$I = \omega C V_0 \cos (\omega t + \frac{\pi}{2})$

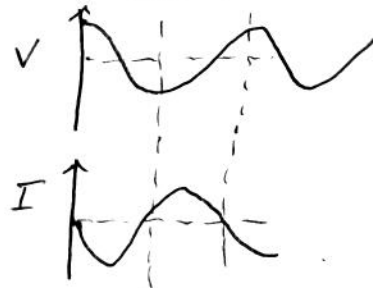So the current leads the voltage by 90° :



same as
 $C \frac{dV}{dt}$

(verifies defn of Z_C)

The ratio of the magnitudes is the reactance,

$|X_C| = \frac{V_0}{I_0} = \frac{1}{\omega C}$ (actually, $X_C = \frac{1}{\omega C}$)

If we instead use an inductor,




$I = \frac{1}{\omega L} \cos (\omega t - \frac{\pi}{2})$, current lags by 90° ,

and $X_L = \omega L$

The circuit on pp. RLC-5, RLC-7 can now be recognized fully as a generalized voltage divider:


Low-Pass
Filter

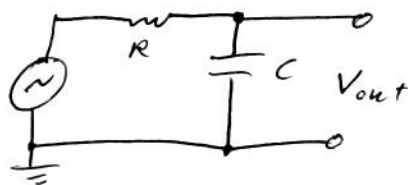

$\hat{V}_{out} = \hat{V}_{in} \frac{Z_C}{R + Z_C}$


$V_{out} = V_{in} \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$

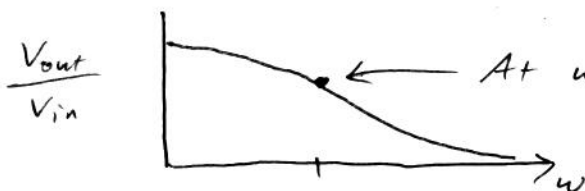phase shift $\phi = -\tan^{-1}(\omega R C)$



At $\omega = \frac{1}{RC}$, $V_{out} = \frac{V_{in}}{\sqrt{2}} = 0.707 V_{in}$

We call this the
"3 dB point"

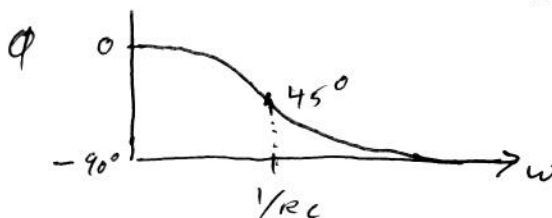


Another Example: capacitors in series & parallel:

$$\frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2}} = \frac{1}{Z} = Z_1 + Z_2$$

$$= \frac{1}{i\omega C_1} + \frac{1}{i\omega C_2}$$

$$= \frac{1}{i\omega} \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = \frac{1}{i\omega C_{eq}}$$
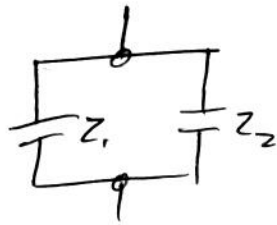
$$\Rightarrow \boxed{\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}}$$



$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2}$$


$$i\omega C_{eq} = i\omega (C_1 + C_2),$$

$$\boxed{C_{eq} = C_1 + C_2}$$

Superposition

But remember, this is for sine wave excitation.

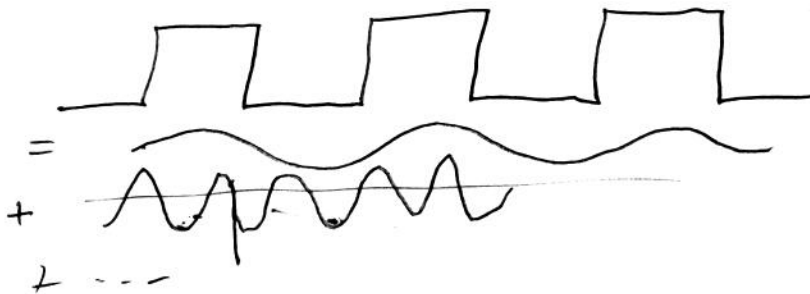For a general wave would use Fourier theorem--



Then superpose to get general solution.



For $V_0 e^{i\omega t}$, $\hat{V}_1 = \frac{Z_c}{R + Z_c} \hat{V}_0 = \frac{\frac{1}{i\omega C}}{R + \frac{1}{i\omega C}} \hat{V}_0$

for V_{dc} , $\hat{V}_{02} = V_{dc}$

So $\hat{V} = V_{dc} + \frac{1}{1 + i\omega RC} \hat{V}_0$

$V = \text{Re} \left(V_{dc} + \frac{1}{1 + i\omega RC} \hat{V}_0 e^{i\omega t} \right)$

$= V_{dc} + \text{soln at } \omega.$

Power in sinusoidally driven ac circuits:

In real notation,

$$P = IV = \operatorname{Re}(\hat{I}) \operatorname{Re}(\hat{V})$$

For a device with impedance Z ,

$$\hat{V} = V_0 e^{i\omega t}, \quad \hat{I} = \frac{V_0}{Z} e^{i\omega t} = \frac{V_0}{|Z| e^{i\phi}} e^{i\omega t}$$

$$\text{So } P = \frac{V_0^2}{|Z|} \cos \omega t \cos(\omega t - \phi)$$

The average power over a cycle is then

$$\langle P \rangle = \frac{V_0^2}{|Z|} \frac{1}{2\pi/\omega} \int_0^{2\pi/\omega} \cos \omega t \cos(\omega t - \phi) dt$$

$$\neq \operatorname{Re}(\langle \hat{I} \hat{V} \rangle)$$

$$\langle P \rangle = \frac{V_0^2}{|Z|} \frac{\omega}{2\pi} \int \left(\underbrace{\frac{1}{2} \cos(2\omega t - \phi)}_{=0 \text{ over cycle}} + \frac{1}{2} \cos \phi \right) dt$$


$$\boxed{P_{\text{avg}} = \frac{1}{2} \frac{V_0^2}{|Z|} \cos \phi = \frac{V_{\text{rms}}^2}{|Z|} \cos \phi}$$

power factor = 0 for pure L, C

In general, only real Z's consume power.
This can alternatively be written as

$$\boxed{P_{\text{avg}} = \frac{1}{2} \operatorname{Re}(V_0^* I_0)} = \frac{1}{2} \operatorname{Re}\left(\frac{V_0^* V_0}{Z}\right) = \frac{|V_0|^2}{2} \operatorname{Re} \frac{1}{Z} \\ = \frac{|V_0|^2}{2|Z|} \cos \phi \text{ as above}$$

Example: LR high-pass filter

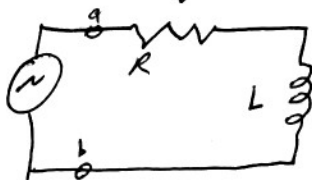

Input impedance seen by source is
 $Z = R + i\omega L$

(Re, Im parts equal at $\omega_0 = \frac{R}{L}$)

$$|Z| = \sqrt{R^2 + \omega^2 L^2}, \quad \phi = \tan^{-1} \frac{\operatorname{Im}(Z)}{\operatorname{Re}(Z)} = \tan^{-1} \frac{\omega L}{R}$$

Note that $\cos(\tan^{-1} a) = 1/\sqrt{1+a^2}$

$$\text{so } \cos \phi = 1/\sqrt{1 + \frac{\omega^2 L^2}{R^2}} = \frac{R}{\sqrt{R^2 + \omega^2 L^2}}$$

$$\text{Thus } P_{\text{avg}} = \frac{V_0^2 R}{2} \frac{1}{R^2 + \omega^2 L^2} \text{ approaches } \frac{V_0^2}{2R} \text{ as } \omega \rightarrow 0$$

Incidentally, it's easy to show that in general,

$$\operatorname{Re} z_1 \operatorname{Re} z_2 = \frac{1}{2} (\operatorname{Re} (z_1 z_2) + \operatorname{Re} (z_1^* z_2)).$$

↑
For a sinusoid, cycle average = 0

Often power is measured in Decibels:

In comparing two powers P_1 and P_2 ,

$$\text{dB} = 10 \log_{10} \frac{P_2}{P_1} \quad \text{or} \quad 20 \log_{10} \frac{V_2}{V_1}$$

$\sim$ amplitudes

3 dB = factor of 1.995... $\approx$ factor of 2 in power


6 dB $\approx$ factor of 2 in voltage

Normally used as a relative measure, but can also be referred to a standard reference point -

{ dBm are dB relative to 1 mW into 50 ohms
{ dBV are dB relative to 1 Volt rms

Decibels are very widely used in describing filters and response curves

For an RC low-pass,

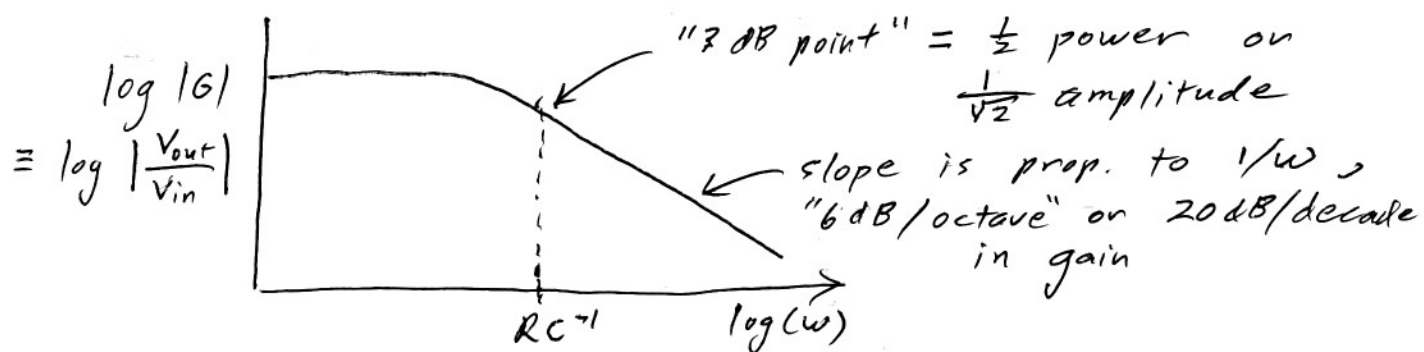

Note that in a plot of power, slope would be larger on graph, but would still be described as 6 dB/octave --- dB always refers to power.

These "Bode plots" are used extensively to study response and ϕ shifts.

The GdB/octave is characteristic of any single-pole network, (whose ~~the~~ $\hat{V}_{out}/\hat{V}_{in}$ transfer function has a single zero in the denominator). It also inevitably has a phase shift of the type we've described! (complex analyticity).


High-pass filter:



$$\frac{V_{out}}{V_{in}} = \frac{R}{R + \frac{1}{i\omega C}}$$

$$I_{out} = \frac{V_{out}}{R} = V_{in} \frac{i\omega C}{1 + i\omega RC}$$

LC & LRC circuits ; resonance

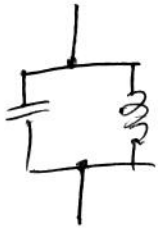

$$Z_{eff} = \frac{1}{\frac{1}{Z_C} + \frac{1}{Z_L}} = \frac{1}{i\omega C + \frac{1}{i\omega L}}$$

$$= \frac{i\omega L}{1 - \omega^2 LC}$$


So V, I are out of phase by $\pm 90^\circ$

and $|Z| = \frac{\omega L}{1 - \omega^2 LC} \rightarrow \infty$ as $\omega \rightarrow \frac{1}{\sqrt{LC}} = \omega_0$

Series LC similar, but $|Z| \rightarrow 0$ as $\omega \rightarrow \frac{1}{\sqrt{LC}} = \omega_0$.

More realistic is LRC circuit without the discontinuity.

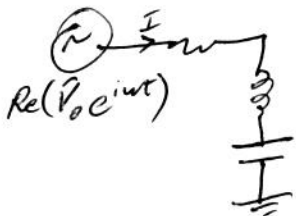As example, look at series case. Monitor I or $V_R = IR$





$$Z_{eff} = R + i\omega L + \frac{1}{i\omega C}$$

$$\hat{I} = \frac{\hat{V}_0}{R + i\omega L + \frac{1}{i\omega C}}$$

Writing $Z = |Z|e^{i\phi}$, $|Z| = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$
 $\phi = \tan^{-1} \frac{\omega L - \frac{1}{\omega C}}{R}$

and $I = \frac{V_0}{|Z|} \cos(\omega t - \phi)$

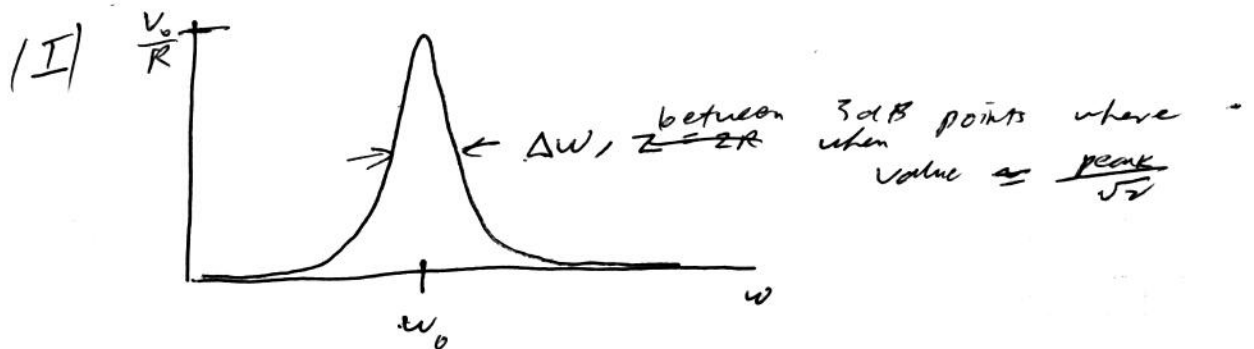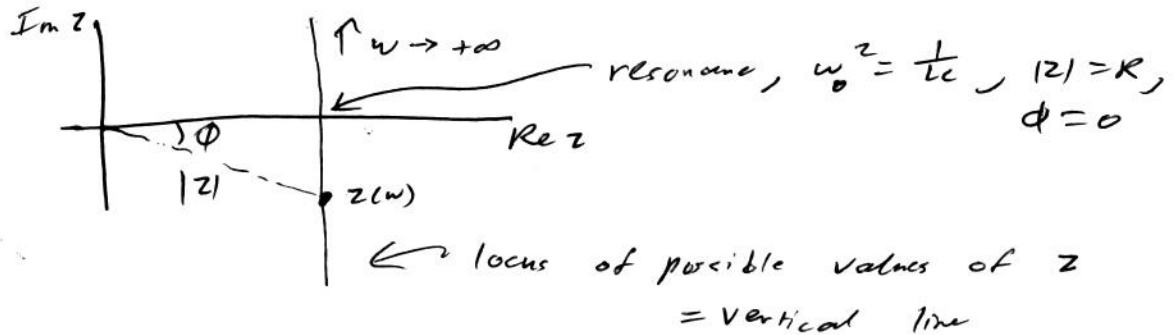


"Quality" factor $Q = \frac{\omega_0}{\Delta\omega} = \frac{f_0}{\Delta f}$, measured between 3-dB points where $|I| = \frac{1}{\sqrt{2}}$ of peak
 $= \omega_0 L / R$

LC parallel RLC is similar (it's in lab!)


Here we get $\omega_0^2 = \frac{1}{LC}$ again, but
 $Q = \frac{R}{L\omega_0}$ (see next page for details)

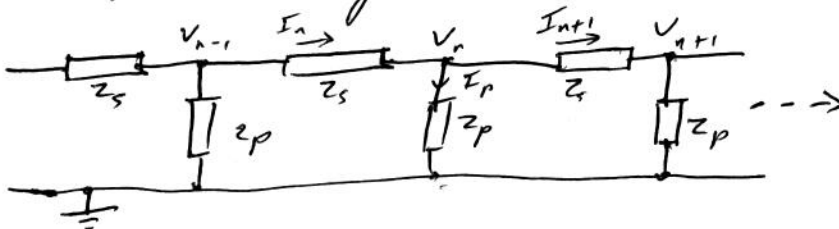Transmission Line: To expand horizons, consider an LC string:



Assume Z_s, Z_p are L's & C's. Then $\text{Re}(Z) = 0$
 and there's no power dissipation.

Detail: Q of RLC in lab 3;

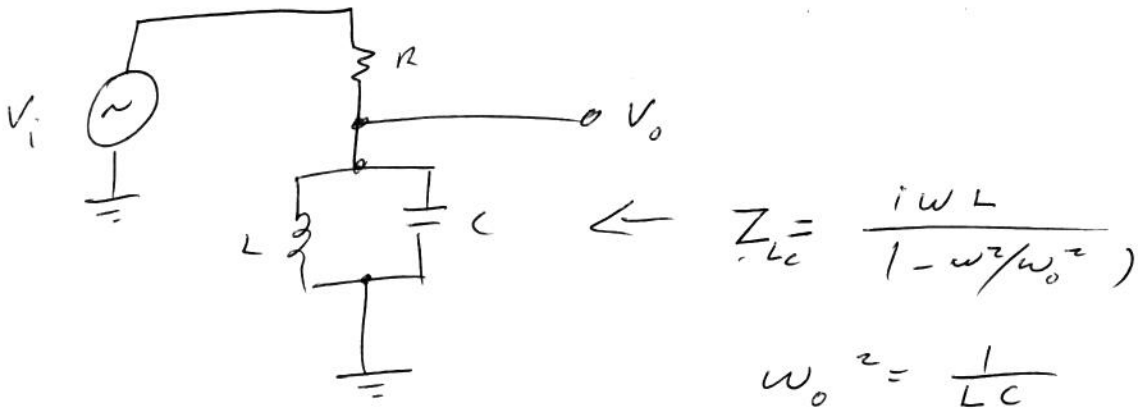

$$G = \frac{V_o}{V_i} = \frac{Z}{R+Z} = \frac{i\omega L}{i\omega L + R\left(1 - \frac{\omega^2}{\omega_0^2}\right)}$$

$$|G|^2 = \frac{\omega^2 L^2}{\omega^2 L^2 + \left(R\left(1 - \frac{\omega^2}{\omega_0^2}\right)\right)^2}$$

$$= 1 \quad \text{at} \quad \omega = \omega_0$$

$$= \frac{1}{2} \quad \text{when} \quad \omega L = R\left(1 - \frac{\omega^2}{\omega_0^2}\right)$$

$$\frac{1}{2}\text{-power points at} \quad \frac{\omega L}{R} \omega_0^2 = \omega_0^2 - \omega^2$$

$$\text{For } \omega \approx \omega_0, \quad \omega_0^2 - \omega^2 \approx 2\omega_0(\omega - \omega_0), \text{ so}$$

$$\omega - \omega_0 \approx \frac{\omega L}{2R} \omega_0 \approx \frac{L}{2R} \omega_0^2$$

$$\text{Thus } Q = \frac{\omega_0}{2(\omega - \omega_0)} = \frac{R}{L\omega_0} \quad \left(= \frac{1}{Q} \text{ for series RLC.}\right)$$

$$\approx 14 \quad \text{for} \quad \omega_0 = 2\pi(20 \text{ kHz}),$$

$$R = 39 \text{ k}$$

$$L = 22 \text{ mH}$$

We also expect no one stage to be 'special'.

Thus a good guess is,

$$V_n = V_{n-1} e^{i\phi}, \text{ constant } \phi \text{ shift / stage.}$$

(like a standing wave, or pure travelling wave)

Circuit eqns:

$$\textcircled{1} \quad V_{n-1} - V_n = I_n Z_s$$

$$\textcircled{2} \quad I_n - I_{n+1} = I_p = \frac{V_n}{Z_p}$$

$$\textcircled{2} \times Z_s \text{ gives } I_n Z_s - I_{n+1} Z_s = V_n \frac{Z_s}{Z_p}$$

$$\text{from } \textcircled{1}, \quad (V_{n-1} - V_n) - (V_n - V_{n+1}) = V_n \frac{Z_s}{Z_p}$$


$$V_{n-1} + V_{n+1} = \left(2 + \frac{Z_s}{Z_p}\right) V_n$$

$$\text{Substituting } V_n = e^{i\phi} V_{n-1},$$

$$e^{i\phi} + e^{-i\phi} = 2 + \frac{Z_s}{Z_p}$$


$$2 \cos \phi = 2 + \frac{Z_s}{Z_p}$$
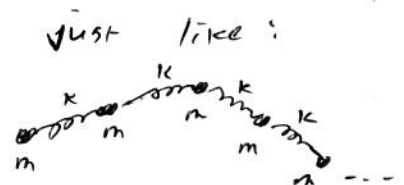
$$\boxed{4 \sinh^2 \frac{\phi}{2} = - \frac{Z_s}{Z_p}}$$



$$\frac{Z_s}{Z_p} = \frac{i\omega L}{1/i\omega C} = \omega^2 LC$$

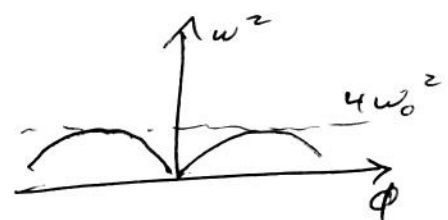
$$\boxed{4 \sinh^2 \frac{\phi}{2} = \frac{\omega^2}{\omega_0^2}}, \quad \omega_0^2 = \frac{1}{LC}$$



Transmits only $\boxed{\omega < 2\omega_0}$

When $\omega > 2\omega_0$, Φ is imaginary $\Rightarrow$ exp. attenuation!

Continuous limit:

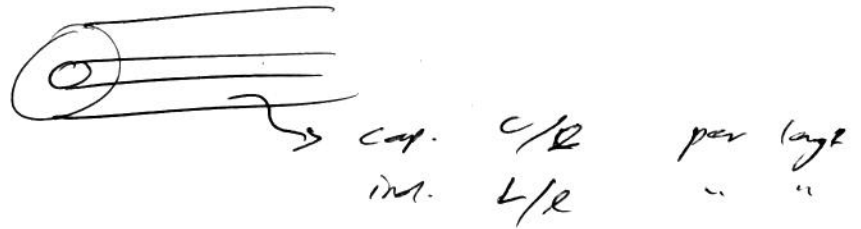

Ratio L/C conserved.

To make it look infinite, terminate with Z_{char} :



$Z = ?$

Well,



$$Z = i\omega L + \frac{1}{i\omega C + \frac{1}{Z}}$$

$$\Rightarrow Z = \frac{i\omega L}{2} + \sqrt{\frac{L}{C} - \left(\frac{\omega L}{2}\right)^2}$$

$\uparrow$ solve for Z $\uparrow$ inductor $\uparrow$ resistor (value depends on ω !)

Cont. limit:



$$Z = \sqrt{L/C}$$

is $\propto$ resistor!



losses infinite!

Trickier -- scope probes:

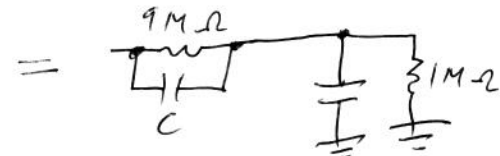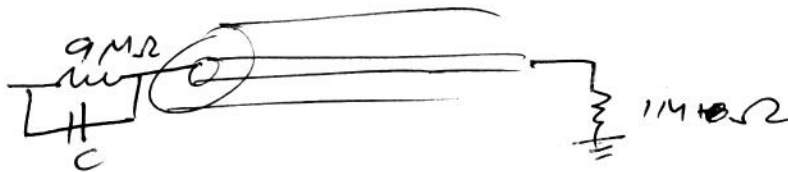

C_{cable} is compensated by a cap. at the scope end of the probe ass'y -- see text. Forms a 10:1 divider at all frequencies!

In a 500 kHz probe, 10-12 components. Deals with L_{cable} , tuning for finite length, etc.