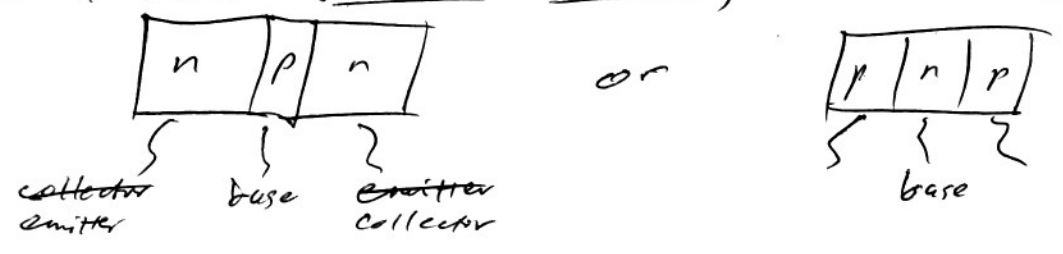


Transistors ("transfer resistors")

We will largely follow Ch. 2 of Horowitz & Hill, not Eggleston.

For a basic junction transistor, structure is




Basic model: $I_C \approx \beta I_B$ typ. ~ 100 , wide range.
 In data sheets, usually written $I_C \approx h_{FE} I_B$

if the following are true (written for npn)

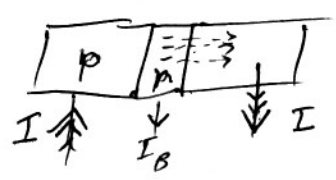- 1) c is more (+) than e
- 2) b-e is conducting, but b-c diode is reverse-biased
- 3) There are max. values for I_C , I_B , V_{CE} , V_{BE} , ... which are not exceeded.

In general terms, e-b conduction injects charge carriers ---




Not same as two diodes ---
 most of E-B internal current continues to the collector.

Can read about physics in other texts; not discuss it

Note: Can get $V_C - V_E$ as low as 0.1 - 0.2 V
Saturation voltage

Emitter follower:


Basic circuit

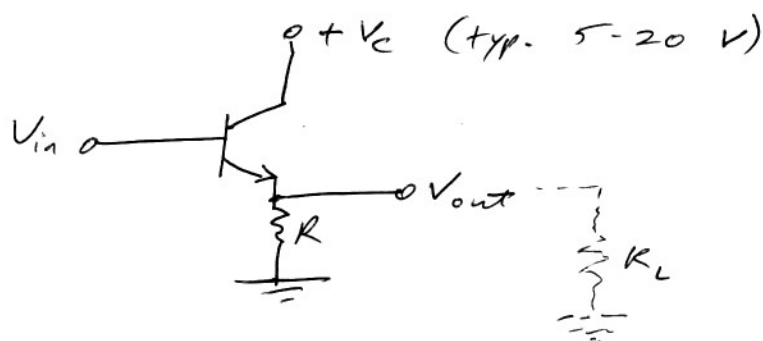

Once biased into conduction at the B-E junction, the transistor acts to preserve the relation

$$V_{in} - V_{out} = V_B - V_E \approx 0.6 \text{ V.}$$

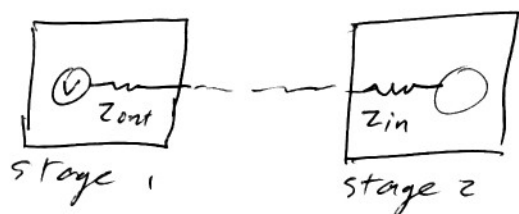Utility: can drive large ~~input~~ output current with a small input current. No voltage gain, but it's an impedance transformer that can have large power gain:



To simplify design, we normally want $Z_{2,in} \gg Z_{1,out}$ (by at least a factor of ten or so; assumes voltage sources.)

To analyze the response to a small change at the input, it's convenient to break up the voltages and currents into two pieces.

Introducing lower-case notation for small changes or ac signals,

$$V_B(t) = V_B^{DC} + v_B(t)$$

$$V_C(t) = V_C^{DC} + v_C(t)$$

$$V_E(t) = V_E^{DC} + v_E(t)$$


likewise $I_B(t) = I_B^{DC} + i_B(t)$, etc.

small change = signal, often time-dependent.

steady-state dc value ("quiescent" or "bias" voltage = operating point)

Can also write as $v_B = \Delta V_B$, etc.

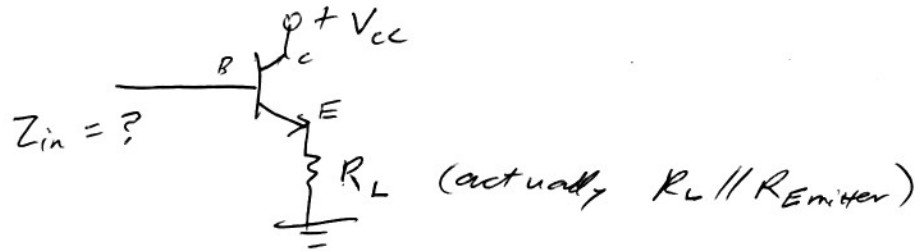Now back to the emitter follower, with our super-simplified model:



$$\textcircled{1} \quad I_E = I_B + I_C \approx I_B (1 + \beta)$$

$$\textcircled{2} \quad \text{Find } Z_{in} = \frac{V_B}{i_B} \text{ for small changes } V_B.$$

$$\text{Since } V_E \approx V_B - 0.6 \text{ V,}$$

$$\Delta V_E = v_E \approx v_B,$$


$$\text{Also, } i_E = \frac{V_E}{R_L} \text{ and from } \textcircled{1}, i_E \approx i_B (1 + \beta)$$

$$\text{So } Z_{in} = \frac{V_B}{i_B} \approx \frac{V_E}{i_E / (1 + \beta)} = \frac{V_E (1 + \beta)}{V_E / Z_L}$$

$$\boxed{Z_{in} \approx R_L (1 + \beta)} \text{ for emitter follower}$$

(increased by up to $\sim 100 \times$!)

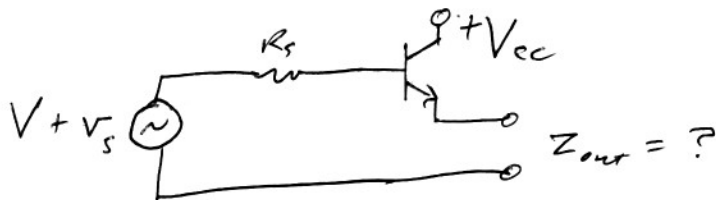There's a similar beneficial effect as viewed from the output:



$$\text{For small changes (ac response), } Z_{out} \equiv \frac{v_{th}}{i_{\text{"short-circuit"}}}$$

$$\text{where } v_{th} = v_E \approx v_s \quad (\text{i.e., Thevenin equivalent } Z)$$


$$\text{and } i_{\text{short-circuit}} \text{ is actually } i_E \text{ with } V_E \text{ fixed at } V_E^{DC}.$$

(i.e., ac short-circuit)

$$\text{Then } i_{s-c} \approx i_B (1 + \beta) = \frac{v_s}{R_s} (1 + \beta) \text{ - and}$$

$$Z_{out} = \frac{v_s}{\frac{v_s}{R_s} (1 + \beta)} \quad \boxed{Z_{out} = \frac{R_s}{1 + \beta}}$$

Summarizing,



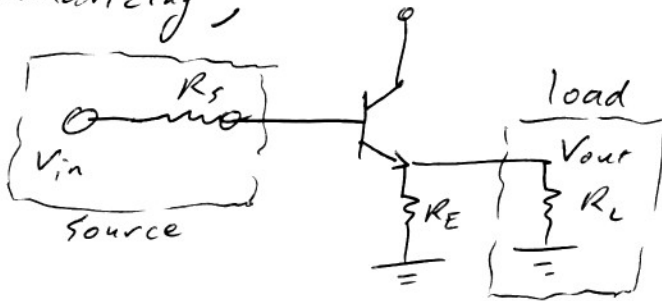


1) $V_{out} \approx V_{in} - 0.6V$


2) $Z_{out} \approx \frac{R_S}{1+\beta} \parallel R_E$ (usually irrelevant)

3) $Z_{in} = (R_L \parallel R_E)(1+\beta)$

Example: improved power supply --- $\approx R_L \beta$ under most conditions.

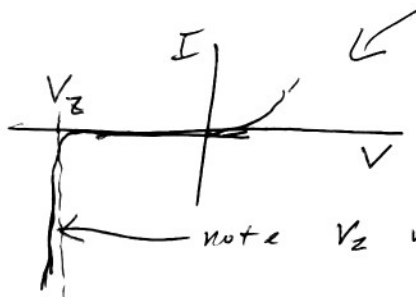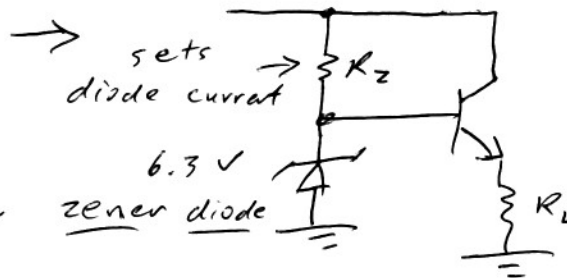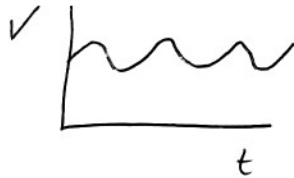note V_Z varies slightly with I_Z

From the perspective of the Zener diode,

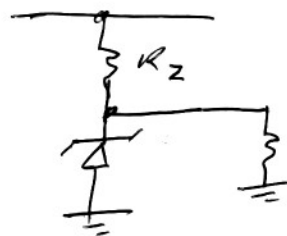

$$Z_{in} = R_L(1+\beta)$$

has reduced effect on I_Z as R_L varies.


$\Rightarrow$ Regulation improves by $\sim$ factor of β compared with circuit without follower.

$\Rightarrow$ Can use much lower current through Zener diode: more thermally stable, does not need high-current ratings.


Biasing: What if input isn't always at $\sim$ a few Volts?



Solution 1: Bipolar power supplies

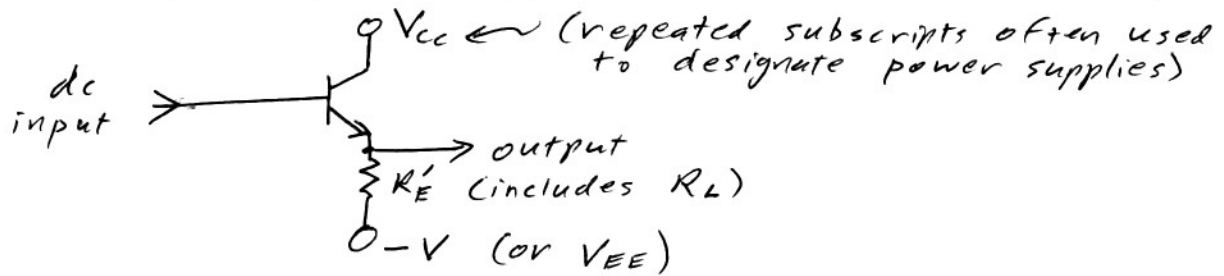

or

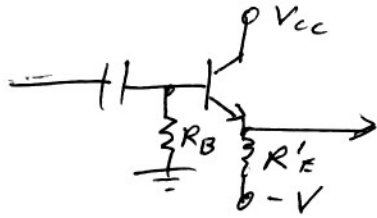


Here R_B supplies base current. To maintain a stable operating point, but avoid loading the input, make $R_B \approx \frac{1}{\beta} Z_{\text{follower}}$

$$\approx \frac{1}{\beta} (\beta + 1) R_E'$$

For $\beta \sim 100$, this yields $Z_{\text{in}} \sim 10 R_E'$.

Solution 2: Biasing circuit, most often a "stiff voltage divider"

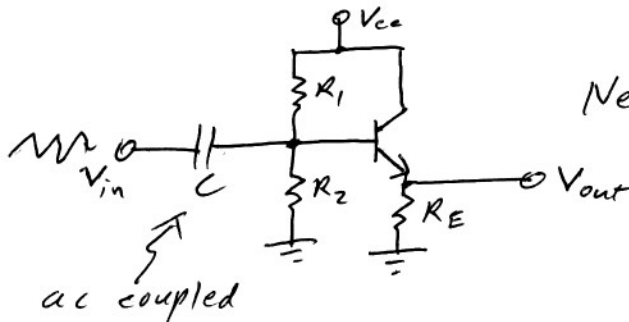Make $Z_{\text{divider}} \ll Z_{\text{driven}} \approx \beta R_E'$



Need $R_1 // R_2 \ll \beta R_E'$

Design process:

① Make $R_{\text{in}} C \gg \text{slowest } \tau_{\text{signal}}$,

where $R_{\text{in}} \equiv R_1 // R_2$, since R_{follower} is large by comparison.

② Make $\frac{R_2}{R_1 + R_2} \sim \frac{1}{2}$ to center range at $V_{cc}/2$.

i.e., pick $R_1 \approx R_2$.

- ③ choose R_E for a small quiescent current, but not so large that you can't drive the load (can omit R_E if load fixed, always connected.)

If we have $V_C = 10V$, $R_E = 10k$,
 then $I = 1mA$ max (ignoring Z_{load}) or $0.5mA$ quiescent.
 Pick $R_1 = R_2 = 10k$; note Z_{in} of transistor is $\sim 100 \times 10k$


If $200Hz$ is lowest input freq., need

$$RC \gg \frac{1}{300(2\pi)}, \text{ or } \frac{10^4}{2} C \gg \frac{1}{2000}$$

$$C \gg 0.1 \mu F \text{ (pick } 4.7 \mu F)$$

(we could make R_1, R_2 larger, but not too large.)


Current source:

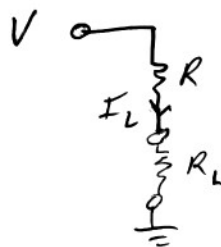

I_L is very dependent on load unless $R \gg R_L$.

$\rightarrow$ poor except at very low current.

Instead use

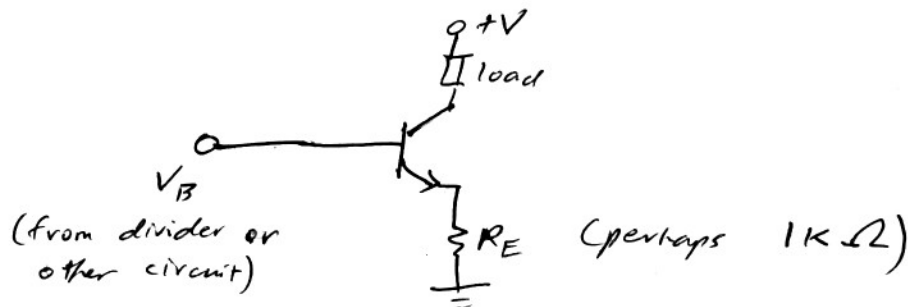


We have $I_C \approx I_E$ if β is large,
 since $I_B = I_C / \beta$.

Also $V_E \approx V_B - 0.6V$, so

$$I_C \approx \frac{V_E}{R_E} \approx \boxed{\frac{V_B - 0.6V}{R_E}} (\approx I_E).$$


Compliance range set by $V_C > V_E + 0.2V$; $V_E = I_E R_E$.
 (Note: $0.2V$ is the sat. volt. drop.)

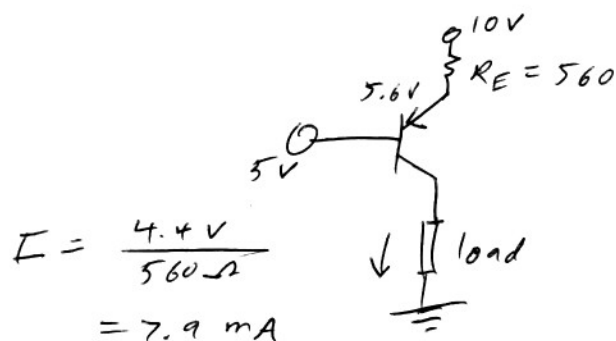While this version sinks current, a pnp variation can source it—



Common emitter amplifier:

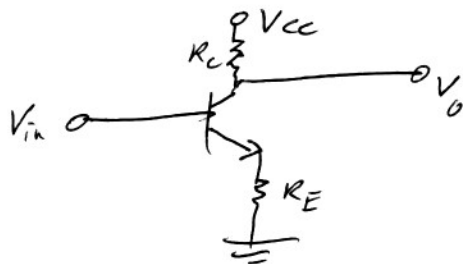How to build a voltage amplifier? One way is to use a current source with a resistor as its load:



Here $V_o = V_c = V_{cc} - I_c R_c$ ① and $I_c \approx I_e = \frac{V_B - 0.6V}{R_E}$ ②

For a small change V_B in the input

$$V_B = V_B^{DC} + v_B,$$

I_c changes by $i_c = \frac{v_B}{R_E}$ per ② and


V_c changes by $v_c = -i_c R_c$ per ①.

Thus $v_c = -v_B \frac{R_c}{R_E} \Rightarrow \text{gain } G = \frac{v_o}{v_{in}} \approx \frac{-R_c}{R_E}$

Should be accurate if β is large and R_E (called 'a' by Eggleston!)

1) Input is a small change in the quiescent operating point, and

2) R_E is not so small that something else limits G (more on this shortly).

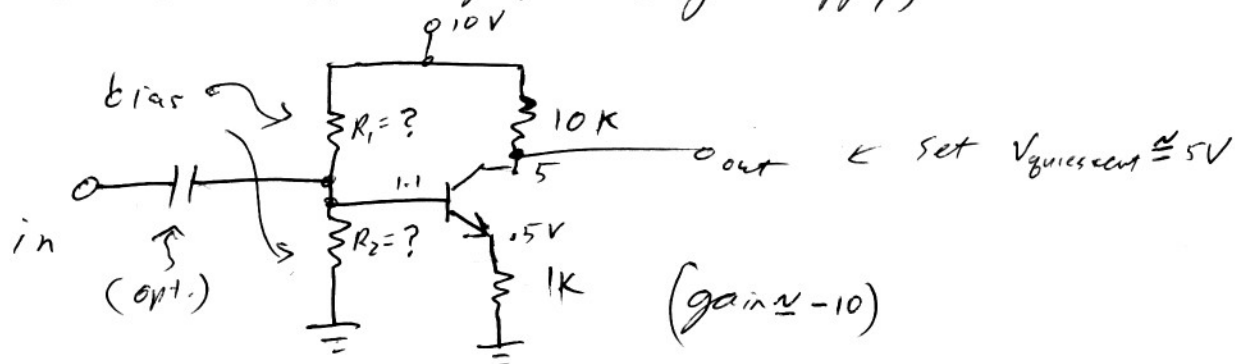Practical common emitter amplifier (single-supply):

Can this be done using 1K and 10K, as shown?

We need output $\sim 5V$ when $V_{in} = 0$, to get max. swing.

To do this, we want 5V drop across 10K, or $I_c^{DC} = 0.5mA$

This requires $V_E \sim 0.5V$ (gives 0.5mA into 1K),

or $V_B^{DC} \sim 1.1V$. So $\frac{R_2}{R_1 + R_2} = \frac{1.1}{10} = \frac{11}{100}$.

What are good values? We need

- 1) High input Z , but
- 2) operating point reasonably independent of input, and especially, of base current.

Impedance looking into base is $\sim R_E \beta$, or around 100K. So we need $R_1 // R_2 \ll 100K$.

A reasonable choice is $R_2 = 10K$, so $R_1 = 80.9K$ would be ideal.

Quiescent current is just 0.5mA, so nothing heats up much.

But max current is only $\sim 1mA$, so not exactly a huge drive here.

Input impedance: $Z_{in} = R_1 // R_2 // (R_E (1 + \beta))$, just under 10K

Output impedance: looking into collector it's $M\Omega$, so result is $Z_{out} = 10K$. (High Z is OK only if load is also high- Z .)

Looking into emitter: ~~low~~ Z
 collector: high Z (current source)

Why can't we make gain arbitrarily high by varying resistor ratios R_C/R_E ? Of course, it's mostly because our transistor model is so bad:

Ebers-Moll eq'n: Improved model (residual problems summarized later.)

Recall for a diode, $I = I_S (e^{\frac{+V}{V_T}} - 1)$.


Zero-order model: take $\Delta V \sim 0.6V$ always.

Not surprisingly, a qualitatively similar situation is a better view for a transistor, too.

Think of circuit in new terms -- as a transconductance amplifier --



$$g_m = \frac{I_{out}}{V_{in}}$$

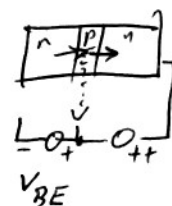

The improved description is:

$$I_E \cong I_S \left(e^{\frac{V_{BE}}{V_T}} - 1 \right)$$

where $V_T = \frac{k_B T}{q} = 25.3 \text{ mV}$ at 20°C , just like diode but with $n=1$.

and I_S = saturation current, varies with transistor and T .

$$\text{So } I_E = I_S \left(\frac{V_{BE}}{V_T} + \frac{1}{2} \left(\frac{V_{BE}}{V_T} \right)^2 + \dots \right)$$

if we also assume $I_B \propto V_{BE}$,
 I_E prop. to I_B ~~for~~ to lowest order.

So we see now that β depends on I_C , T , and also, it turns out, V_{CE} !

Main effect --- There is an effective resistance r_e looking into the emitter, intrinsic to the device.

Intrinsic emitter resistance - for small signals, use E-M model to find $\frac{i_E}{v_{BE}} = \frac{dI_E}{dV_{BE}} \approx I_S \frac{1}{V_T} e^{V_{BE}/V_T}$

Since $e^{V_{BE}/V_T} \gg 1$ in normal use,

$$\frac{i_E}{v_{BE}} \approx \frac{I_E}{V_T} \quad \left(\approx I_S e^{V_{BE}/V_T} \right)$$

Thus the effective resistance is the reciprocal of this,

$$r_e = \frac{v_{BE}}{i_E} \approx \frac{V_T}{I_E}, \text{ or, since } I_C \approx I_E \text{ in most cases,}$$


$$\text{or } \boxed{r_e \approx \frac{25 \Omega}{I_C \text{ (in mA)}} = \frac{0.025 \Omega}{I_C \text{ (in A)}}} \quad (\text{using } V_T \approx 25 \text{ mV})$$

 r_e appears in series with any external impedance.


Secondary consequences: Because I_S varies with T as well as with V_{BE}/V_T , it turns out that for constant I_C , $V_{BE} \propto 1/T$, and it decreases by $\approx 2.1 \text{ mV}/^\circ\text{C}$ for Si transistors. (Thus thermal runaway becomes a concern!)

Effects on our circuits:


i) Emitter follower:

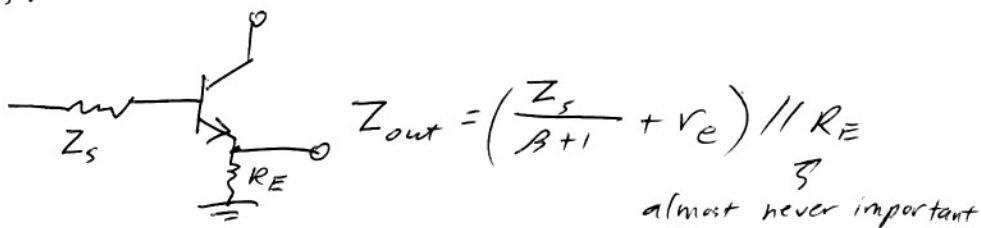

For example,

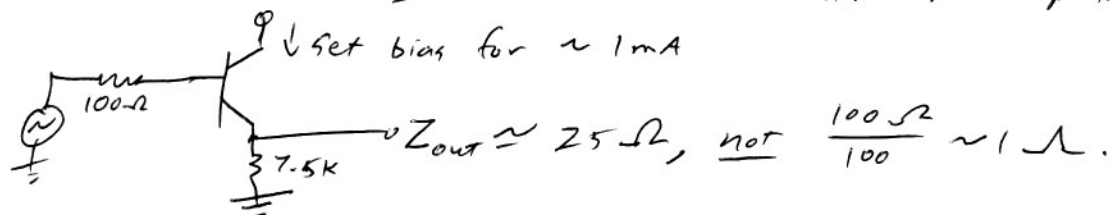

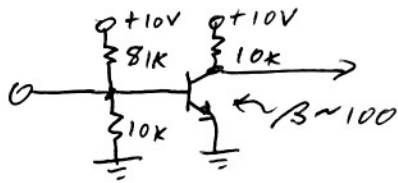2) Common-emitter amplifier — consider grounded emitter:



Gain $\neq \infty$!

At quiescent point, 5V out corresponds to 0.5 mA, so $r_e = 50\Omega$.

$$G = \frac{10k}{50} = 200, \text{ not } \infty.$$

Also, because I_c varies widely with signal, gain varies from 0 to 400 over the full output range!

Further, input impedance βr_e is unstable, and base is very hard to bias — for fixed V_{BE} , I_c will rise tenfold for 30C of heating!


Solutions:

- 1) Add emitter resistors as before with $R_E \gg r_e$, defining quiescent current and limiting gain.
- 2) Bypass emitter resistor, decoupling gain from dc bias.
- 3) Feedback — see Horowitz and Hill.



Other bipolar transistor circuits

Darlington:

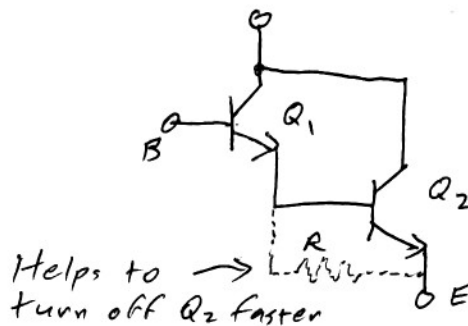


Readily available pre-packaged.

$$\beta \approx \beta_1 \beta_2$$

(but drops at least 1.2V on base)


Another variation is

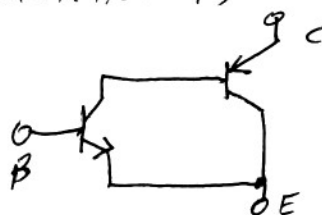

(Behaves as an npn transistor)


Push-pull power amp:

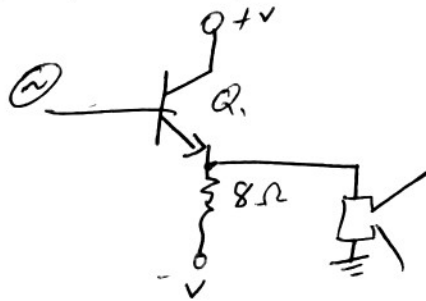It's very inefficient to use a single transistor for high-power applications:



need quiescent current $\geq$ max output current.
resistor, Q_1 both dissipate more power than load.

Instead, try

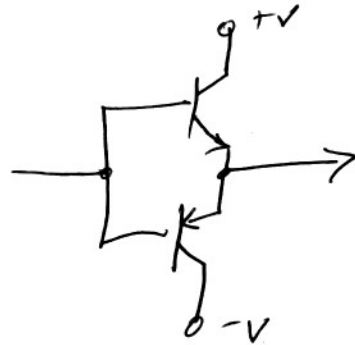


"Class B"

Works OK, but clips near 0V:





So bias it into conduction --

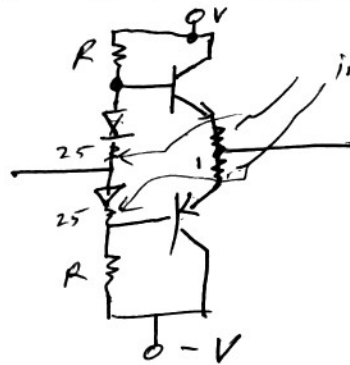

improves thermal stability --
Change in V_{BE} doesn't change quiescent current as quickly,

Saturated switching:

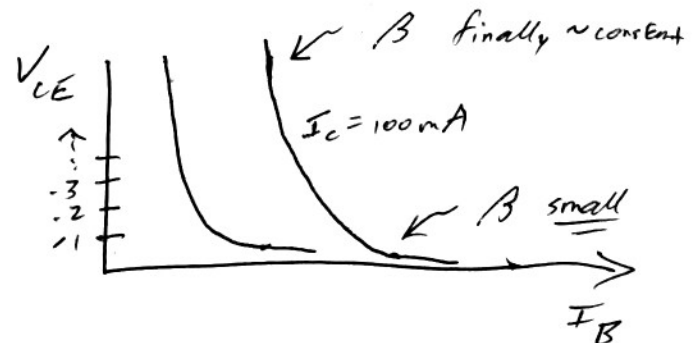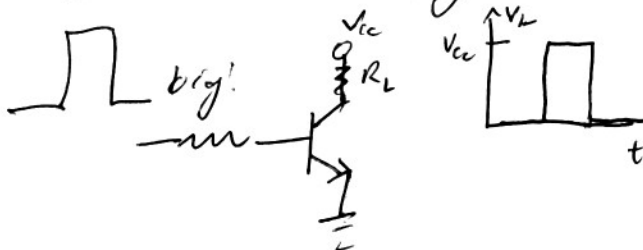

- For high power, use lots of base current (C-B junction is starting to conduct, reducing β .)
- For fast switching, don't turn on or off quite so hard.